

ASSIGNMENT

COURSE CODE:

CSE-2323

COURSE TITLE:

Digital Logic Design

ASSIGNMENT NO:

01

ASSIGNMENT NAME: K-MAP

SUBMITTED TO: Mujibur Rahman Maruf

Assistant Lecturer, Dept. of CSE, HUC.

SUBMITTED BY:

NAME: Iftaher Hossen

ID: C241017

EMAIL:Iftahersayem205@gmail.com

SEMESTER: 3rd

SECTION: 3AM

DEPARTMENT: CSE


SUBMISSION DATE: 11 March 2025

Remarks




31: Simplify the following Bookean function using three Variable map.

a)
$$f(x,y,2) = \sum (3,5,6,7)$$

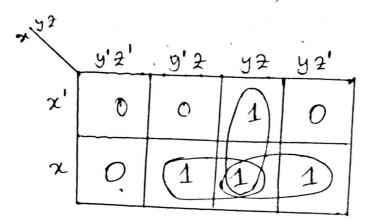

... Simplified function $F = 2x + xy + y^2 = xy + y^2 + 2x$

b)
$$F(A_1B_1C) = \sum (0,2,3,4,6)$$

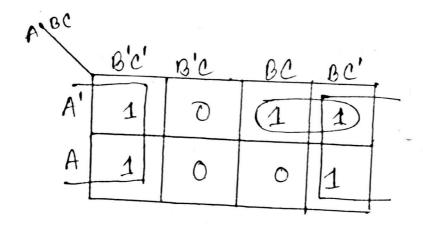

. . Simplified function F = C'+ A'B

3.2 Simplify the following borlean expression using three variable maps.

* A'B+B'c'+B'c'

APC	B'c'	o'c	BC	BC'	
A'	1.1	0	1	1	
A	1	0	0	1	
-		, 1	7		

.. Simplified function F = C' + A'B.

3.3 Simplify the following boolean functions using four variable maps.

$$* f(A_1B_1C_1D) = \sum (4,6,7,15)$$

ABCD					
	C'D'	c'D	CD	CO'	_
A'B'	0	0,	0	0	
A'B	1	0	[1]	1	1
AB	0	0	1	0	
AB'	0	0	0	0	

.. Simplified function F = A'BD' + BCD

WCb	c'o'	C'D	LD	CD'	'
A's'	O	0	1	0	
∧' B	0	0	1	0	
↑ B	Q	1	0	1)	
AB'	0	0	1	0	

.. Simplified exfunction F = CD + ABD + ABC


3:5 simplify the following brodean expression using four rapidable maps.

a) B'D + A'BC' + ABC + ABC'

ABCO	c'o'	1 C'D	en /	CD'
A'g'	0	1	.1	0
A'B	1	1	. 0	0
AB	1	1	0	Ó
AB'	0	1	1	1]
				+

. Simplified function F= B'D+ BC+ AB'C

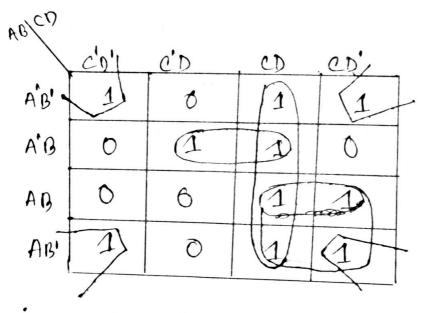b) AB'C + B'C'D' + BCD + ACD' + A'B'C + A'BC'D



:. Simplified function F= CD+A'BD+ ABC+B'D'
B'D'+CD+AC+ A'BD

38 Simplify the following boolean functions using five narriable maps.

9) $f(A_1B_1C_1D_1E) = \sum_{n=0}^{\infty} (0,2,3,4,5,6,9,11,15,16,18,19,23,27,31)$

N DB					BCAF				12.5	
ox Ar	O.E.	D'E	DE	DE'	_ \	DE'	9,E	DE	DE'	
B'C'	1	0	1	1	Вс	1	0	\bigcap	1	
3'C_	1	1	1	1	B°C	\circ	0	1	0	
BC	0	0	1	0	BC	0	0	1	0	
Bc'	0	O	1	0	BC	0	0	1	0	

.: Simplified function F= A' (DE+B'C+B'E')
+ A (DE+B'C'E')

BCDE	D'E'	D'E	DE	DE'
B'C'	1	1	0	0
BC	1	1	0	[1]
BC	0	0	0	1
BC'	0	6	0	1

æ pe	D'E'	D'E	DE.	DE'.
Bet	1	0	0	0
B'C	1	1)	. 0	$\widehat{\mathcal{A}}$
BC	0	0	.0	1
Bei	0	0	0	1)!

= A'B'D'+A'CDE'+A'BDE'+AB'D'E'+AB'CD'+ACDE'+ABDE'

- A'B'D' + A'CDE' + ACDE' + A'BDE' + ABDE' + AB'D'E' + AB'CD'

= A'B'D'+CDE' (A'+A) + BDE' (A'+A)+AB'D'E'+ AB'CD'

= AB'D' + CDE' + BDE' + AB'D'E' + AB'CD'