

DC Generator Video: <https://youtu.be/mq2zjmS8UMI?si=W6HD7kTGB3BiQ8-M>

DC Motor Video Link: https://youtu.be/j_F4limaHYI?si=8z9eP3VPfwBgXJkJ

Commutation

- Commutation is the process of converting the AC voltages and currents in the rotor of a DC machine to DC voltages and currents at its terminals
- When the voltage reverses in a loop, the connections of the loop are also switched to keep the polarity of the terminal voltage the same
- Increasing the number of loops on the rotor, we can improve our approximation to perfect DC voltage
- Commutator segments are usually made out of copper bars and the brushes are made of a mixture containing graphite to minimize friction between segments and brushes

Example 26.3. A shunt generator delivers 450 A at 230 V and the resistance of the shunt field and armature are $50\ \Omega$ and $0.03\ \Omega$ respectively. Calculate the generated e.m.f.

Solution. Generator circuit is shown in Fig. 26.46.

Current through shunt field winding is

$$I_{sh} = 230/50 = 4.6\text{ A}$$

Load current $I = 450\text{ A}$

$$\begin{aligned}\therefore \text{Armature current } I_a &= I + I_{sh} \\ &= 450 + 4.6 = 454.6\text{ A}\end{aligned}$$

Armature voltage drop

$$I_a R_a = 454.6 \times 0.03 = 13.6\text{ V}$$

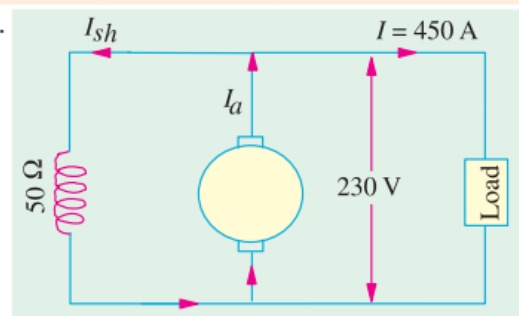


Fig. 26.46

$$\begin{aligned}\text{Now } E_g &= \text{terminal voltage} + \text{armature drop} \\ &= V + I_a R_a\end{aligned}$$

$\therefore$ e.m.f. generated in the armature

$$E_g = 230 + 13.6 = 243.6\text{ V}$$

Example 29.21. A 250-V shunt motor runs at 1000 r.p.m. at no-load and takes 8A. The total armature and shunt field resistances are respectively $0.2\ \Omega$ and $250\ \Omega$. Calculate the speed when loaded and taking 50 A. Assume the flux to be constant. (Elect. Engg. A.M.Ae. S.I. June 1991)

Solution. Formula used : $\frac{N}{N_0} = \frac{E_b}{E_{b0}} \times \frac{\Phi_0}{\Phi}$; Since $\Phi_0 = \Phi$ (given); $\frac{N}{N_0} = \frac{E_b}{E_{b0}}$

$$I_{sh} = 250/250 = 1\text{ A}$$

$$E_{b0} = V - I_{a0} R_a = 250 - (7 \times 0.2) = 248.6\text{ V}; E_b = V - I_a R_a = 250 - (49 \times 0.2) = 240.2\text{ V}$$

$$\therefore \frac{N}{1000} = \frac{240.2}{248.6}; N = 9666.1\text{ r.p.m.}$$