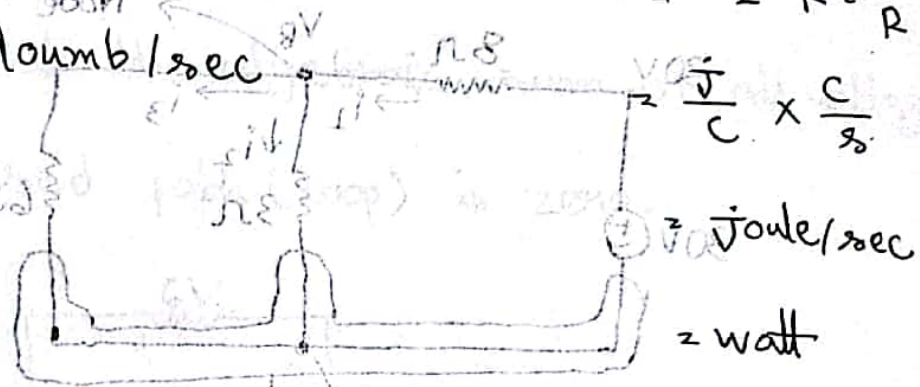


$$V = \text{joule / coulomb}$$

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$I = \text{coulomb / sec}$$



Ohm's law:

Ohm's law states that the voltage across a resistor is directly proportional to the current flowing through the resistor.

$$V \propto I \quad \frac{0-8V}{8} = \left(\frac{1}{8} + \frac{1}{2} + \frac{1}{5} \right) \cdot 8V \quad \text{PRO}$$


$$\therefore V = IR$$

$$I = 8V \quad \therefore$$

$$I \propto V$$

$$\text{or, } I = GV$$
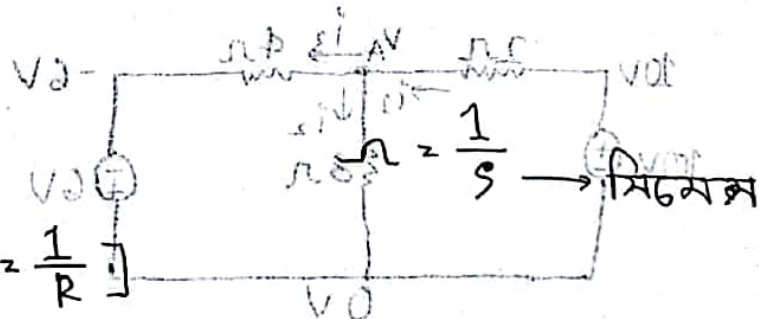
$$\therefore I = \frac{V}{R} \quad [G = \frac{1}{R}]$$



$$\frac{0-8V}{8} = I \quad \frac{2+8V}{8} = I \quad G \rightarrow \text{Conductance}$$


$$P \rightarrow \text{Power}$$

$$P = IV$$

⊞ KCL (Kirchhoff's Current Law):

$$\sum I = 0$$

Sum of all current = 0

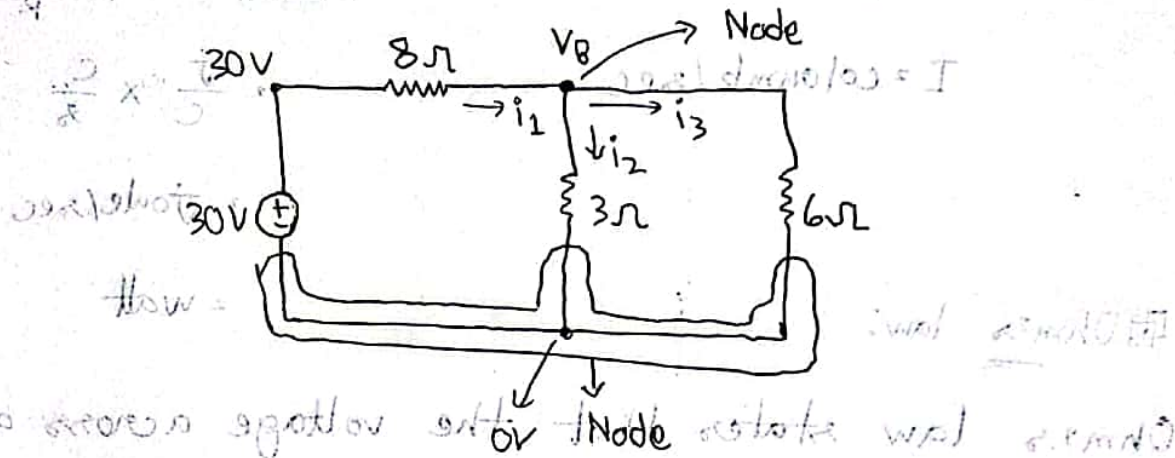


At node B, $i_1 = i_2 + i_3$ (KCL)

$$\text{or, } \frac{30 - V_B}{8} = \frac{V_B - 0}{3} + \frac{V_B - 0}{6}$$

$$\text{or, } V_B \left(\frac{1}{3} + \frac{1}{6} + \frac{1}{8} \right) = \frac{30}{8}$$

$$\therefore V_B = 6$$

#

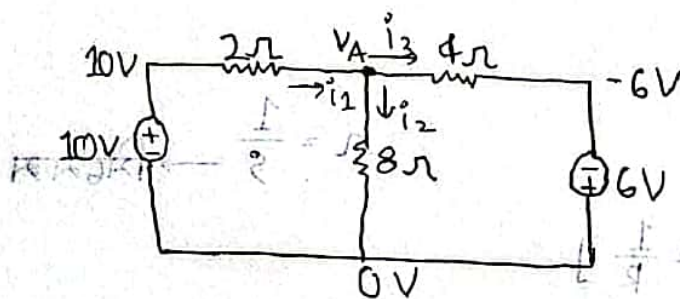


$$i_1 = \frac{10 - V_A}{2} \quad i_3 = \frac{V_A + 6}{4} \quad i_2 = \frac{V_A - 0}{8}$$

$$i_1 = i_2 + i_3$$

$$\therefore V_A = 4$$


KVL (Kirchhoff's Voltage Law):

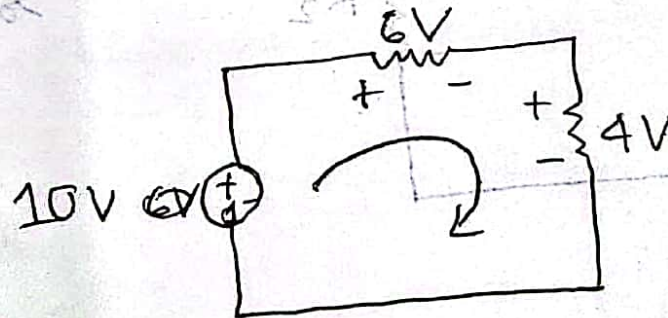KVL states that the algebraic sum of all voltages around a closed path (loop) is zero.



$$+6V + 4V - 10V = 0$$

□ Voltage Divider Rule (VDR):

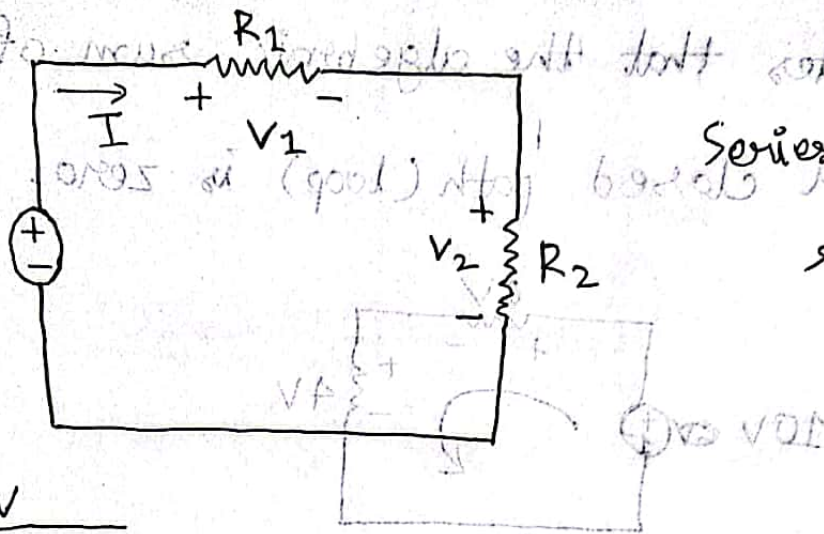

Series $\therefore$ Current same.

$$I = \frac{V}{R_1 + R_2}$$


$$0 = V - V_1 + V_2 +$$

$$V_1 = IR_1$$

$$V_1 = \frac{V}{R_1 + R_2} R_1$$

$$\therefore V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V$$

Current Divider Rules (CDR):

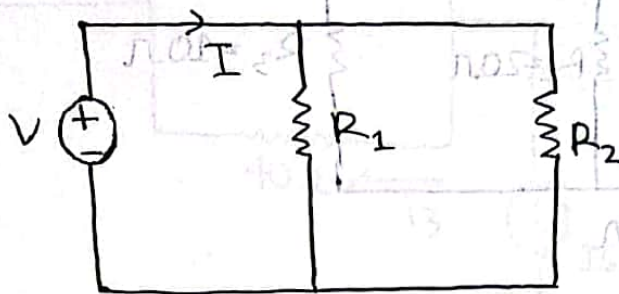

Parallel & Voltage same.

$$I = \frac{V}{R_{eq}}$$

$$\left[\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$I_1 = \frac{V}{R_1}$$

$$\therefore R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{I R_{eq}}{R_1}$$

$$I_1 = I \cdot \frac{R_2}{R_1 + R_2}$$

$$I_1 = I \cdot \frac{R_2}{R_1 + R_2}$$

$$I_1 = I \cdot \frac{R_2}{R_1 + R_2}$$

$$\therefore I_1 = I \left(\frac{R_2}{R_1 + R_2} \right)$$

$$I_2 = I \left(\frac{R_1}{R_1 + R_2} \right)$$

$$I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$


$$V_1 = I R_1$$

$$V_2 = I R_2$$

$$V = I R$$

$$V = I R$$

$$V = I R$$

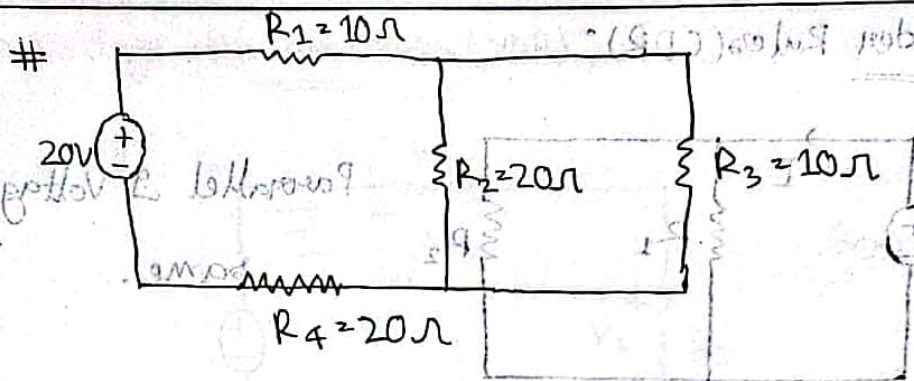

$$R_T = 36.67 \Omega$$

$$V = 20V$$

$$I = \frac{V}{R}$$

$$V = 20 \cdot 0.454A = I_1 = I_4$$

$$I_2 = \frac{R_3}{R_3 + R_2} I$$

$$= 0.1818A$$

$$I_3 = \frac{R_2}{R_2 + R_3} I$$

$$= 0.3636A$$

$$V_1 = IR_1$$

$$= 0.454V$$

$$V_2 = I_2 R_2$$

$$= 3.636V$$


$$= V_3$$

$$V_4 = IR_4$$

$$= 0.454 \times 20$$

$$= 10.908V$$


#

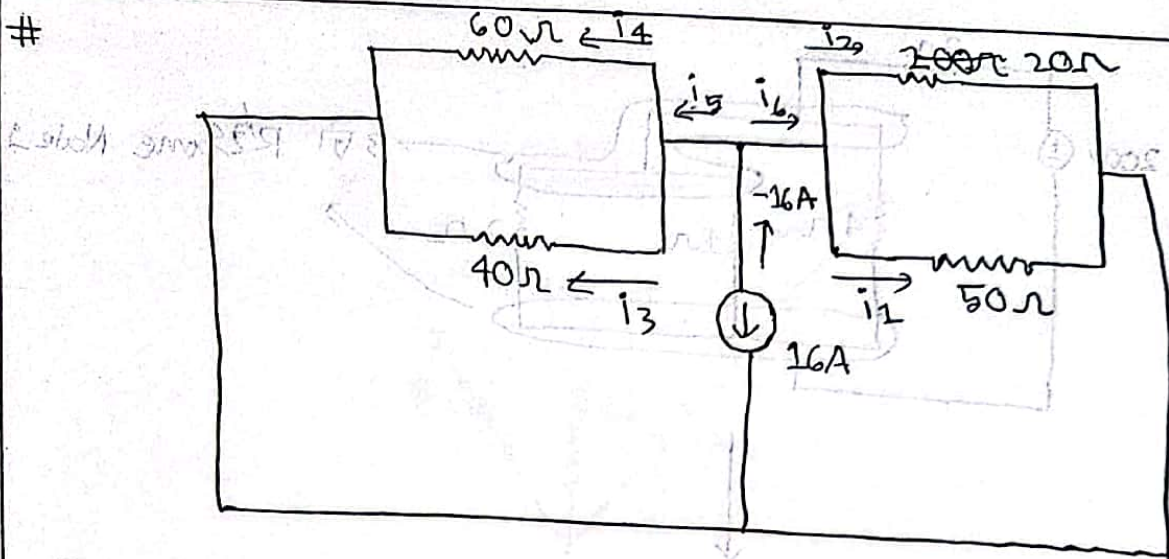

$$I = -16A$$

$$I_6 = \frac{24}{24+40} (-16)$$

$$= -6$$

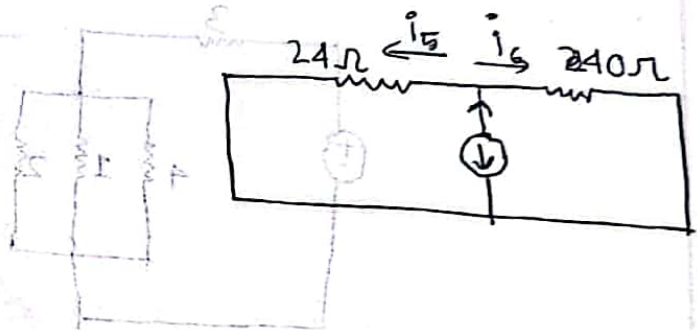

$$I_5 = -10$$

$$I_4 = \frac{40}{40+60} (-10)$$



$$= 4$$

$$I_3 = -6$$

$$I_2 = \frac{50}{50+20} (-6)$$

$$I_1 = \frac{20}{50+20} (-6)$$

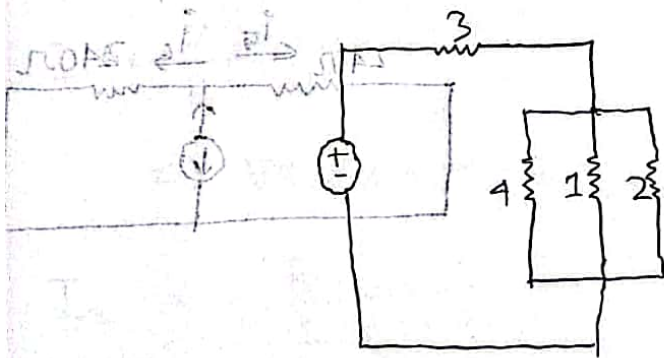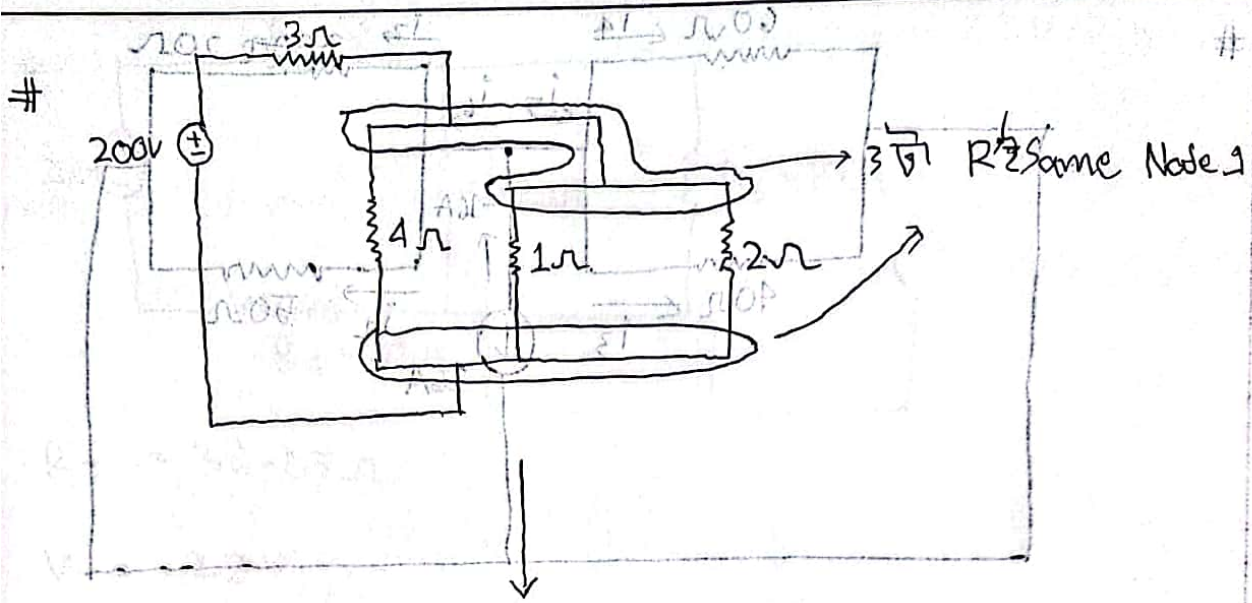$V \oplus \rightarrow$ Independent Voltage Source
 $I \uparrow \rightarrow$ Independent Current Source



$$A_2 I = I$$

$$I_1 = \frac{A_1}{0.5 + 1.0} = I$$

$$I = I$$

$$I_2 = -10$$

$$I_3 = \frac{0.4}{0.5 + 1.0} = I$$

$$I = I$$


$$I_4 = -I$$

$$I_5 = \frac{2.0}{0.5 + 1.0} = I$$

$$I_6 = \frac{5.0}{0.5 + 1.0} = I$$

H.W. $V \leftarrow I$ Voltage source
 $I \leftarrow I$ Current source

Y $\rightarrow$ Δ :

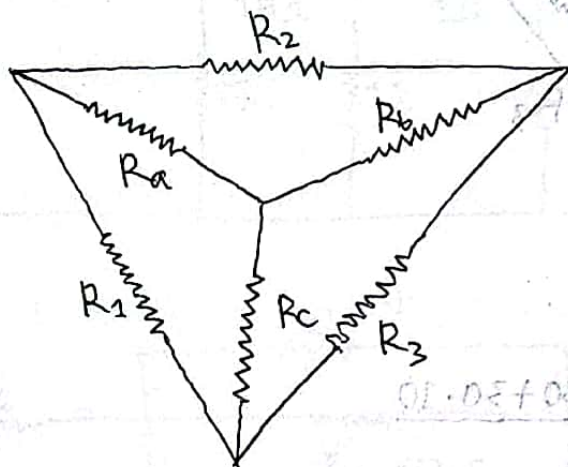

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$


$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$\Delta \rightarrow$ Y:


$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$
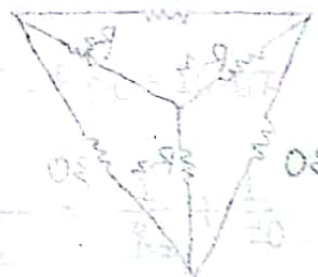
$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$



#

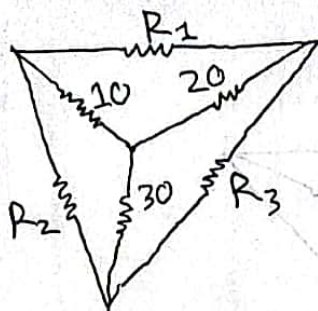

Ans.


$$R_1 = \frac{10 \cdot 20 + 20 \cdot 30 + 30 \cdot 10}{30}$$

$$= \frac{1100}{30}$$

$$R_2 = \frac{1100}{20}$$

$$R_3 = \frac{1100}{10}$$

#

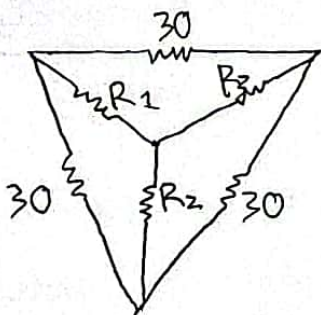


$$R_1 = \frac{30 \times 30}{30 + 30 + 30} = \frac{900}{90}$$

$$R_2 = \frac{900}{90}$$

$$R_3 = \frac{900}{90}$$

Y → Δ

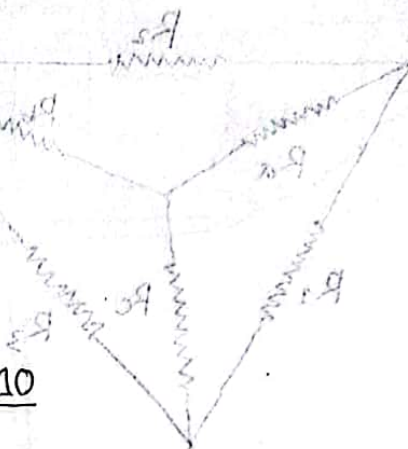

$$R_1 = \frac{R_2 R_3 + R_3 R_1 + R_1 R_2}{R_2}$$

$$R_2 = \frac{R_1 R_2 + R_2 R_3 + R_1 R_2}{R_1}$$



$$R_3 = \frac{R_1 R_2 + R_2 R_3 + R_1 R_2}{R_3}$$

Y → Δ

$$R_1 = \frac{R_2 R_3}{R_2 + R_3 + R_1}$$

$$R_2 = \frac{R_1 R_3}{R_1 + R_3 + R_2}$$
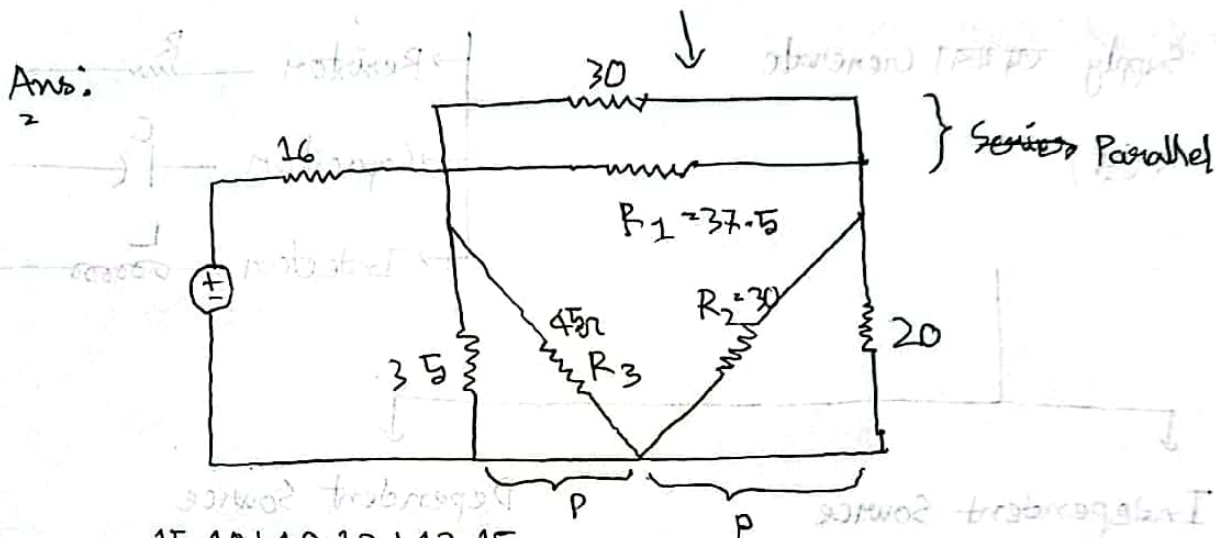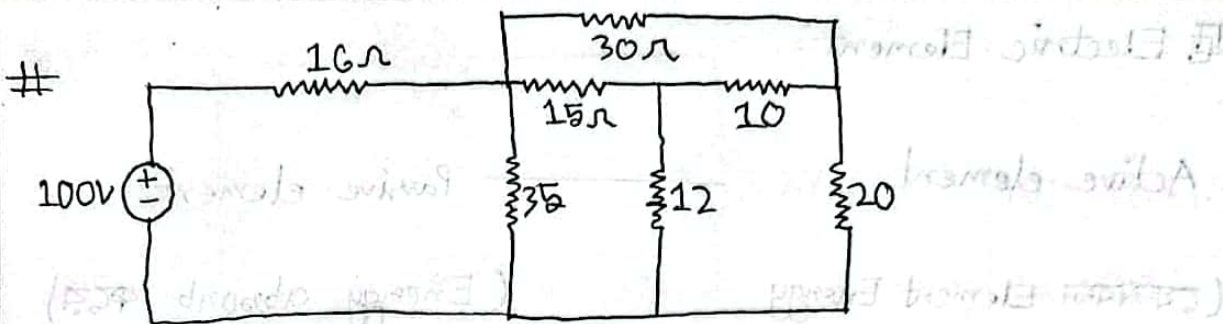
$$R_3 = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$



$$R_1 = \frac{15 \cdot 10 + 10 \cdot 12 + 12 \cdot 15}{12} = 37.5$$

$$R_2 = \frac{450}{15} = 30$$

$$R_3 = \frac{450}{10} = 45$$

$$\frac{1}{R_{P1}} = \frac{1}{30} + \frac{1}{37.5}$$

$$\therefore R_{P1} = 16.67$$

$$\frac{1}{R_{P2}} = \frac{1}{R_2} + \frac{1}{20}$$

$$\therefore R_{P2} = 12$$

$$\frac{1}{R_{P3}} = \frac{1}{R_3} + \frac{1}{35}$$

$$\therefore R_{P3} = 19.6875$$

$$R_s = R_{P1} + R_{P3} = 31.7$$

$$\frac{1}{R_p} = \frac{1}{R_{P1}} + \frac{1}{R_s}$$

Electric Element:

Active element


Passive element

(Generate Element Energy)

(Energy absorb করে)

Supply অথবা Generate

করে)

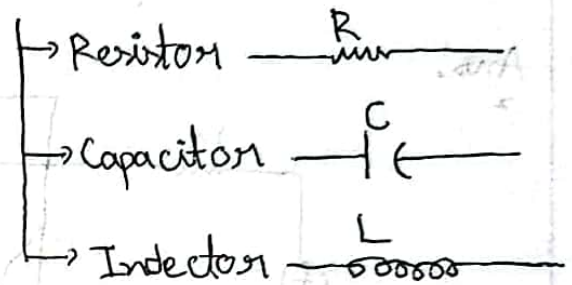

Independent Source

Dependent Source

→ Voltage Source $\oplus$

→ Current Source $\uparrow$

Voltage Source

Current Source

→ Voltage dependent on Voltage source

$\oplus 2V_0$

→ Current dependent on Voltage source

$\uparrow 2i_0$


→ Voltage dependent on current source

$\oplus xV_0$

→ Current dependent on current source

$\uparrow xi_0$

#

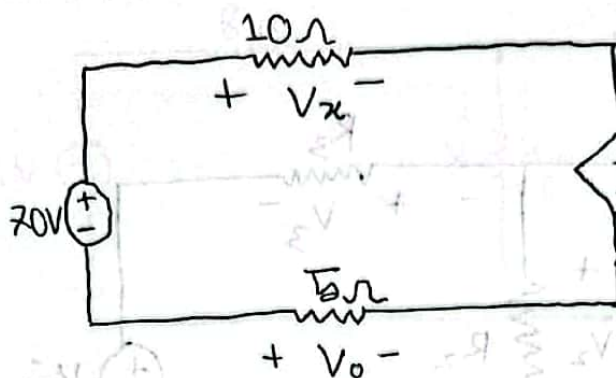

$$V_x = IR = i \cdot 10$$

$$2V_x = 20i$$

$$-70V + V_x + 2V_x - V_0 = 0$$

$$-70 + 10i + 20i + 5i = 0$$


$$\therefore i = 2A$$

$$\therefore V_x = 20$$


$$\therefore V_0 = -10 \quad [-V_0 = 5i \therefore V_0 = -5i]$$

(If you want to find the voltage across the dependent source, you can use KVL)

(current is 2A, voltage is 20V)

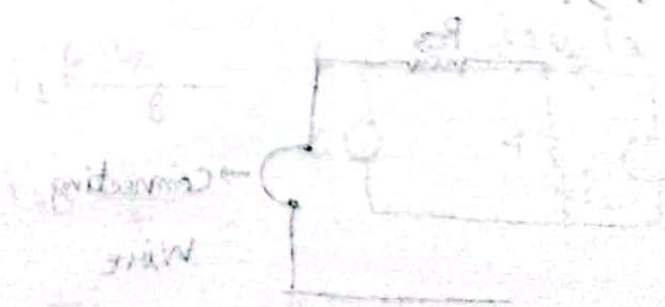

Superposition Theorem:

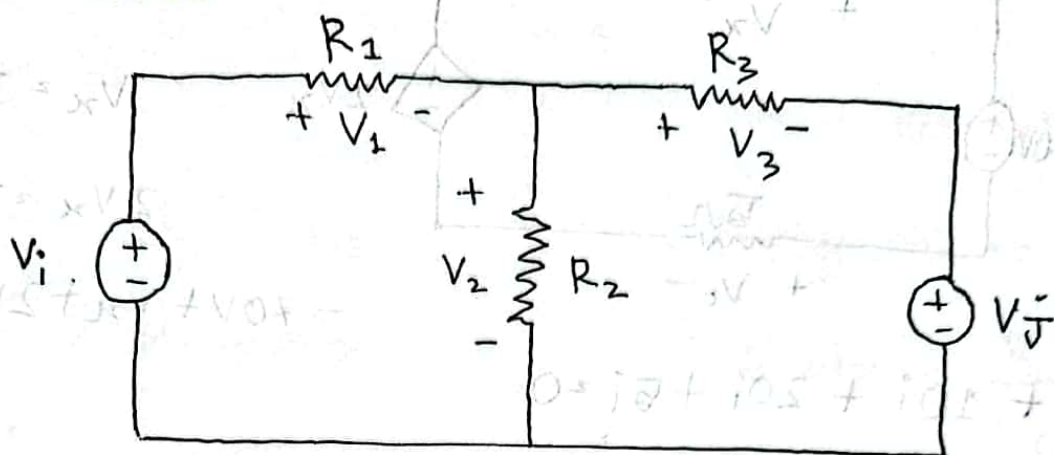


$$V_2 = V_2' + V_2''$$

$\downarrow$
 V_j वाद दिहय
 V_i वाद दिहय


Inactive


- Voltage Source (Short करा / तार दिहय यूँडा करा)
- Current " (Open)

V.S.:


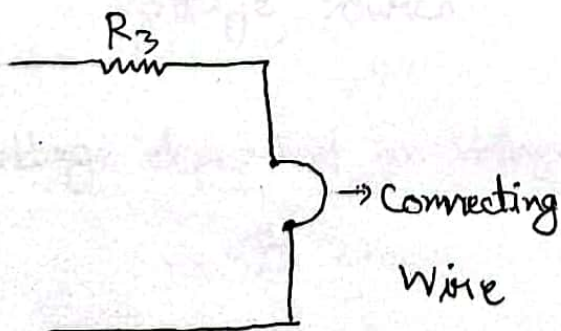


C.S.:

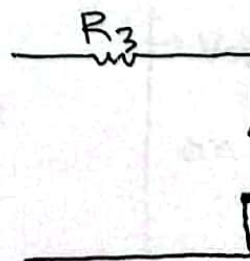

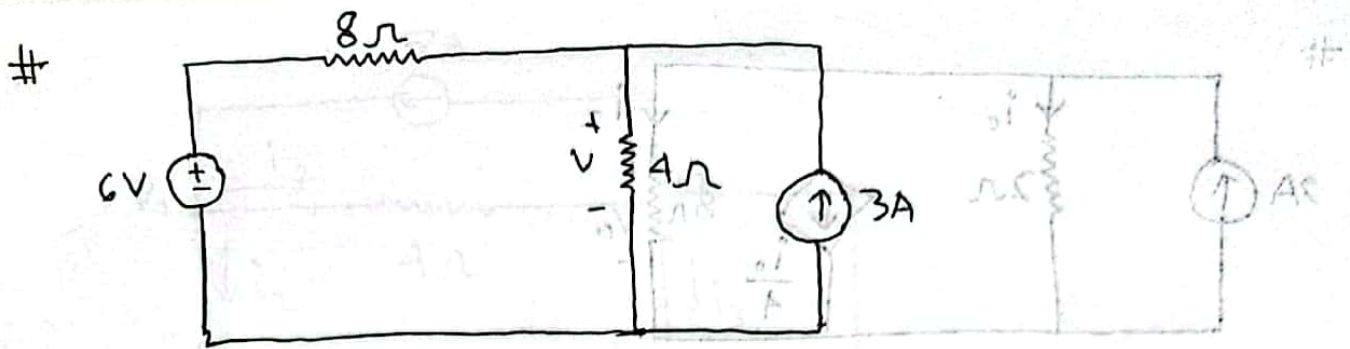

Ans:

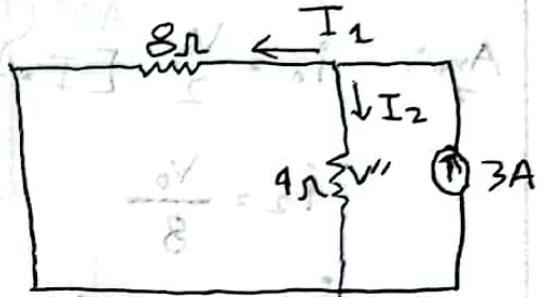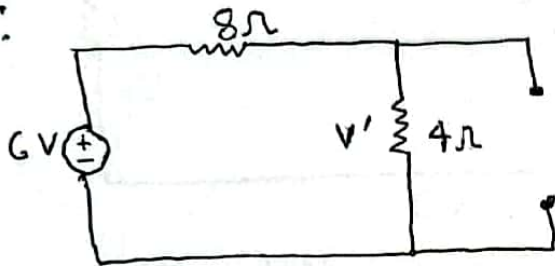

With VDR and CDR:

$$V' = \frac{4}{4+8} \times 6$$

$$\approx 2V$$

$$V'' = I_2 R_2$$

$$= 2 \times 4$$

$$= 8V$$


$$\therefore V = V' + V''$$

$$\approx 10V$$

With KCL:

$$i_1 = \frac{6 - V_A}{8}$$


$$i_2 = \frac{V_A - 0}{4}$$

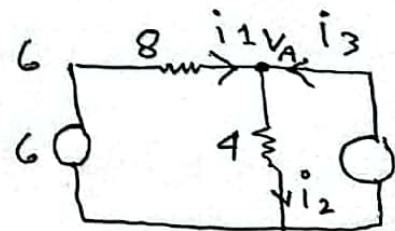

$$i_1 + i_3 - i_2 = 0$$

$$\text{or, } \frac{6}{8} - \frac{V_A}{8} + 3 - \frac{V_A}{4} = 0$$

$$\therefore V_A = 10V$$

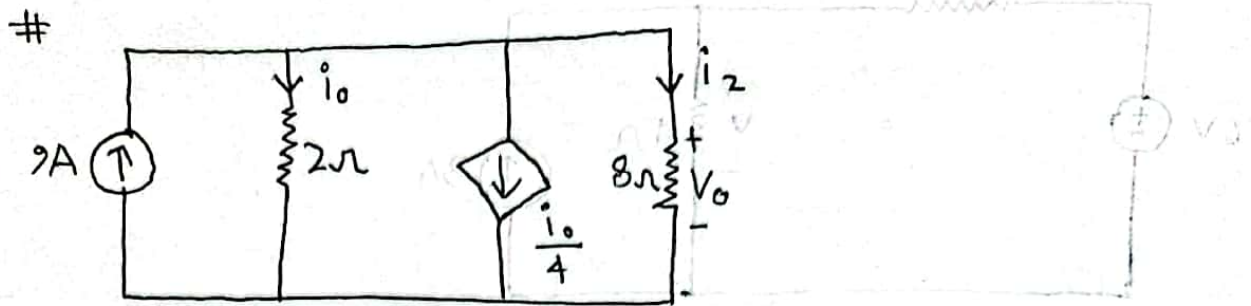

Ans: $i_o = \frac{V_o}{2} \left[I = \frac{V}{R} \right]$

$i_2 = \frac{V_o}{8}$

$i_o + \frac{i_o}{4} + i_2 = 9$

on, $i_o + \frac{i_o}{4} + \frac{V_o}{8} = 9$

on, $i_o + \frac{i_o}{4} + \frac{2i_o}{8} = 9 \left[i_o = \frac{V_o}{2} \therefore V_o = 2i_o \right]$

on, $i_o \left(1 + \frac{1}{4} + \frac{1}{4} \right) = 9$

$\therefore i_o = 6A$



$\frac{4V}{8} = \frac{1}{8}$
 $\frac{0.4V}{1} = \frac{1}{1}$


$0 = 5i - 1i + \frac{1}{8}$

$0 = \frac{4V}{8} - 1 + \frac{1}{8} - \frac{1}{8}$

$10V = 4V \therefore$

#

(A1.8) #

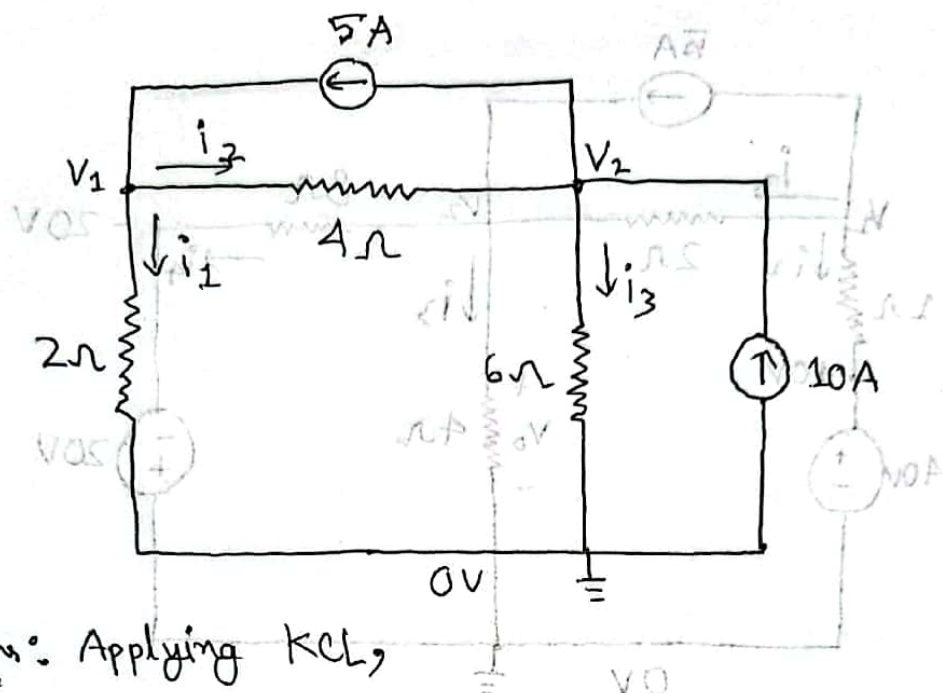

Ans: Applying KCL,

$$i_1 = \frac{V_1 - 0}{2} \quad i_2 = \frac{V_1 - V_2}{4} \quad i_3 = \frac{V_2 - 0}{6}$$

$$i_1 + i_2 = 5$$

$$i_2 - i_3 + 10 - 5 = 0$$

$$\text{or, } \frac{V_1}{2} + \frac{V_1 - V_2}{4} = 5$$

$$\text{or, } \frac{V_1}{4} - \frac{V_2}{4} - \frac{V_2}{6} = -5$$


$$\therefore V_1 \left(\frac{1}{2} + \frac{1}{4} \right) - V_2 \cdot \frac{1}{4} = 5$$

$$\text{or, } V_1 \cdot \frac{1}{4} - V_2 \left(\frac{1}{4} + \frac{1}{6} \right) = -5$$

$$\therefore V_1 = 13.333V$$

$$\therefore V_2 = 20V$$

(3.14)

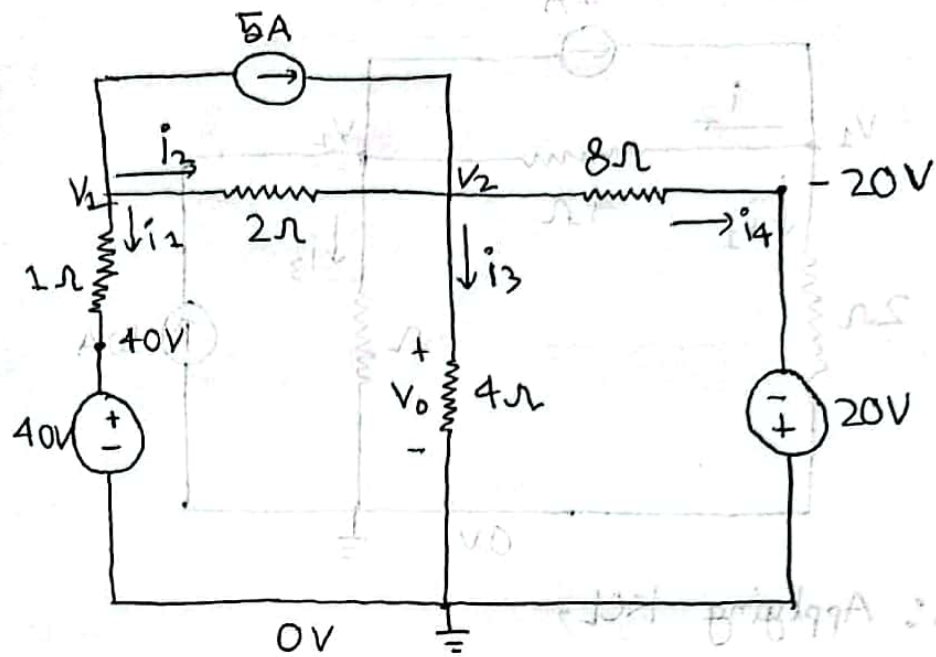

$$i_1 = \frac{V_1 - 40}{1}$$

$$i_2 = \frac{V_1 - V_2}{2}$$

$$i_3 = \frac{V_2 - 0}{4}$$

$$i_4 = \frac{V_2 + 20}{8}$$

$$i_1 + i_2 + 5 = 0$$

$$i_2 + 5 - i_3 - i_4 = 0$$

$$\text{or, } \frac{V_1}{1} - 40 + \frac{V_1 - V_2}{2} - \frac{V_2}{2} = -5$$

$$\text{or, } \frac{V_1}{2} - \frac{V_2}{2} + 5 - \frac{V_2}{4} - \frac{V_2}{8} - \frac{20}{8} = 0$$

$$\therefore V_1 \left(1 + \frac{1}{2}\right) - V_2 \cdot \frac{1}{2} = 35$$


$$\therefore V_1 \cdot \frac{1}{2} - V_2 \cdot \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8}\right)$$

$$= \frac{20}{8} - 5$$

$$\therefore V_1 = 30V$$

$$\therefore V_2 = 20V$$

#

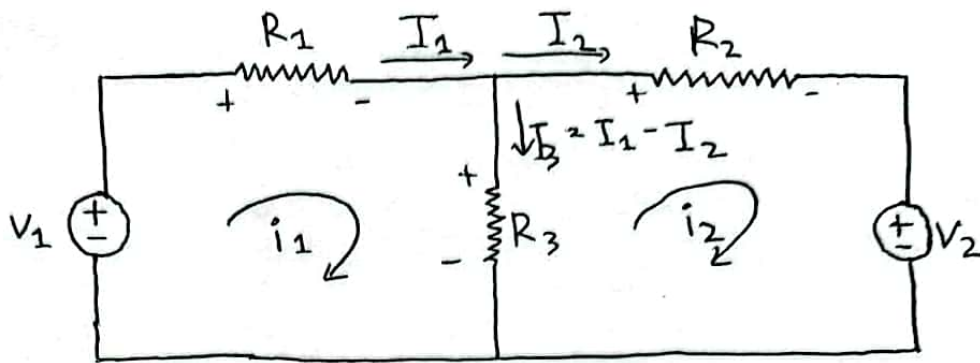


$$\text{Ans: } -V_1 + I_1 R_1 + I_1 R_3 - I_2 R_3 = 0$$

$$\therefore I_1 R_1 + I_1 R_3 - I_2 R_3 = -V_1$$

Loop-2:

$$\therefore -I_1 R_3 + I_2 R_2 + I_2 R_3 = -V_2$$

(3.5)

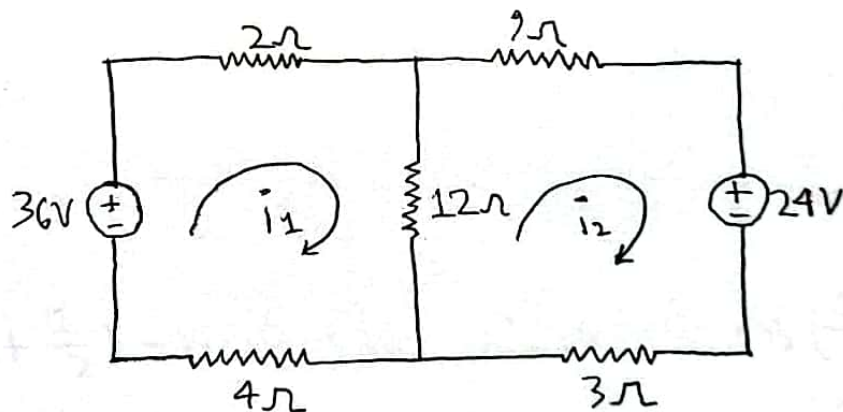

$$i_1(2+12+4) - i_2(12) = 36 \quad [\text{Loop } i_1]$$


$$-i_1(12) + i_2(3+12+9) = -24 \quad [\text{Loop } i_2]$$

— o —

$$i_1(\text{মোট রোধ}) - i_2(\text{কমন রোধ}) = \text{ডোল্টেজ} \quad \text{--- (i)}$$

$$-i_1(\text{কমন রোধ}) + i_2(\text{মোট রোধ}) = \text{ডোল্টেজ} \quad \text{--- (ii)}$$

#

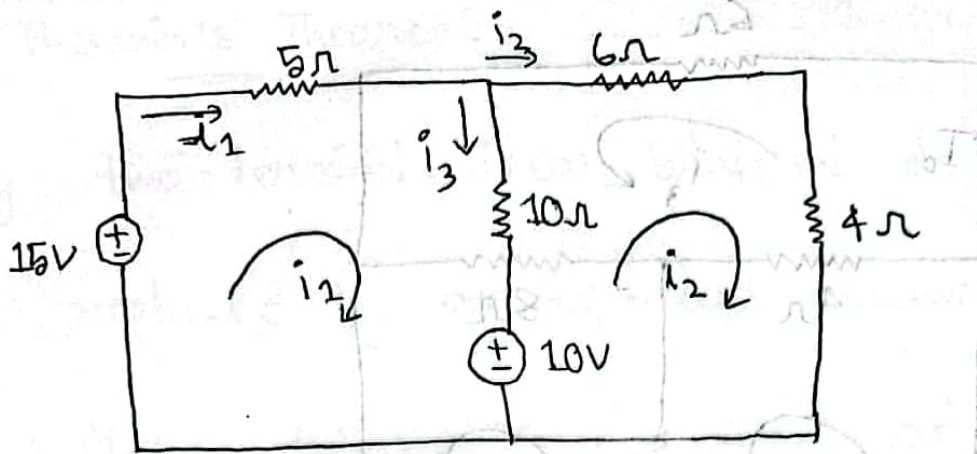


$$i_1(5+10) - i_2(10) = 15 - 10$$

$$-i_1(10) + i_2(10+6+4) = 10$$

$$\therefore i_1 = 1A$$

$$\therefore i_2 = 1A$$

Ex(3.2)

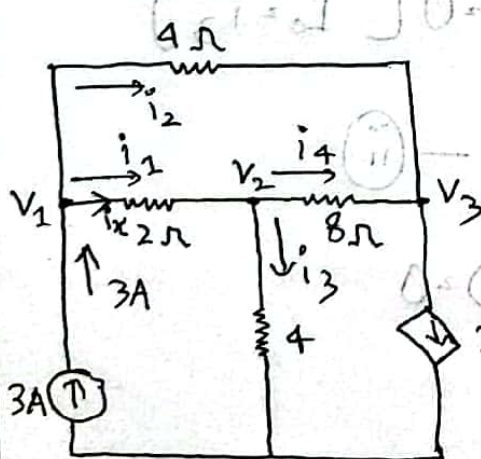

$$i_1 = i_x = \frac{V_1 - V_2}{2}$$

$$i_2 = \frac{V_1 - V_3}{4}$$

$$i_3 = \frac{V_2}{4}$$

$$i = V_2 - V_3$$

$$\textcircled{1} \quad 0 = i_1 - i_2 - i_3 = 0$$

$$i_1 + i_2 = 3$$

$$\therefore V_1 \left(\frac{1}{2} + \frac{1}{4} \right) - V_2 \cdot \frac{1}{2} - V_3 \cdot \frac{1}{4} = 3$$

$$\textcircled{2} \quad 0 = i_1 - i_3 - i_4 = 0$$

$$\therefore V_1 \left(\frac{1}{2} \right) - V_2 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) + V_3 \cdot \frac{1}{8} = 0$$

$$\textcircled{3} \quad i_4 + i_2 - 2i_1 = 0 \quad [2i_x = 2i_1]$$


$$\therefore V_1 \left(\frac{1}{4} - 1 \right) + V_2 \left(\frac{1}{8} + 1 \right) + V_3 \left(-\frac{1}{8} - \frac{1}{4} \right) = 0$$

$$V_1 = 4.8V$$

$$V_2 = 2.4V$$

$$V_3 = -2.4V$$

#(3.6)

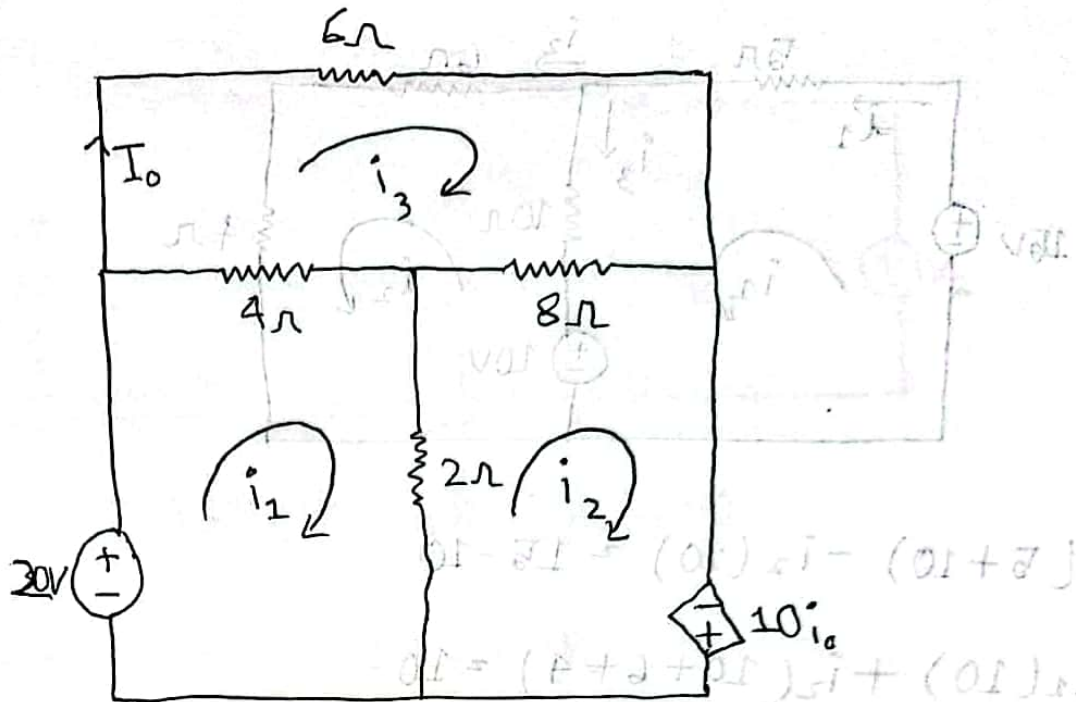

$$i_1(2+4) - i_2(2) - i_3(4) = 30 - 20$$

$$\therefore 6i_1 - 2i_2 - 4i_3 = 10 \quad \text{--- (i)}$$

$$-i_1(4) + i_2(2+8) - i_3(8) - 10i_3 = 0 \quad [I_0 = i_3]$$

$$\therefore -4i_1 + 10i_2 - 8i_3 - 10i_3 = 0 \quad \text{--- (ii)}$$

$$-i_1(4) - i_2(8) + i_3(4+8+6) = 0$$

$$\therefore -4i_1 - 8i_2 + 18i_3 = 0 \quad \text{--- (iii)}$$


$$i_1 = -3.21A$$

$$i_2 = -9.643$$

$$i_3 = -5$$

Theremin's Theorem:

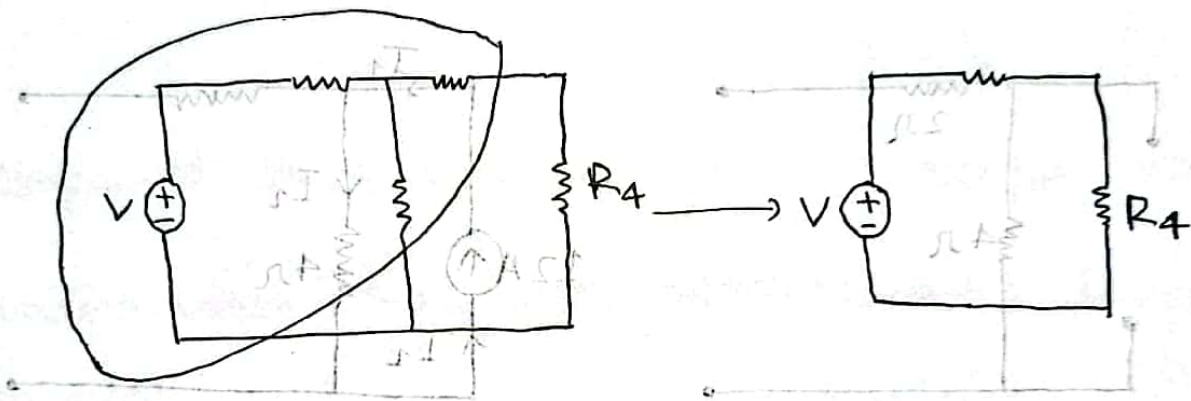Any two-terminal, linear bilateral dc network can be replaced by an equivalent circuit consisting of a voltage source and a series of resistors.



$$V_{TH} = 18V$$


$$R_{TH} = 2 + 2 = 4\Omega$$

$$4.5\Omega = R_4$$

$$V_{AB} = 18V$$

Theremin's Theorem

Ans

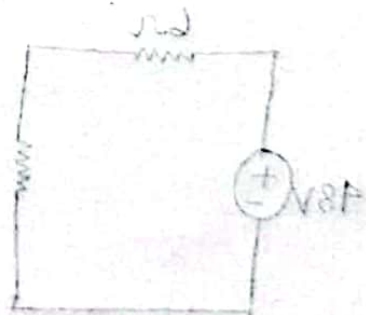

Source transformation

Theremin's Theorem





$$\frac{V}{R_{TH}} = I$$


$$\frac{18}{4} = I$$

$$4.5 =$$

#

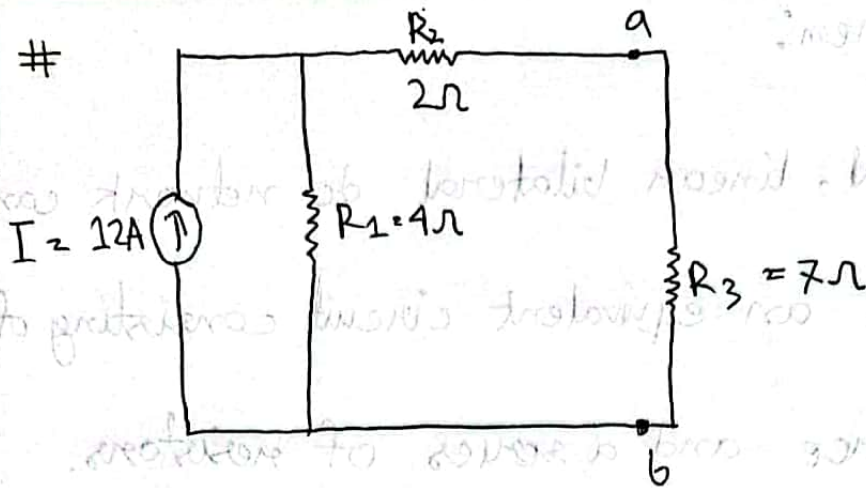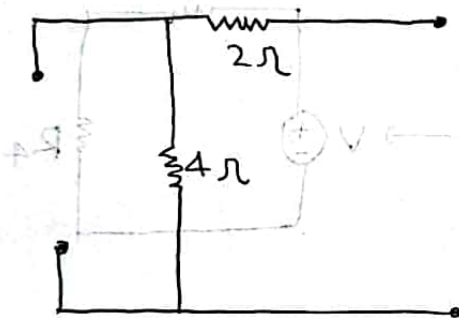Ans:
2


$$R_{TH} = 2 + 4 = 6\Omega$$

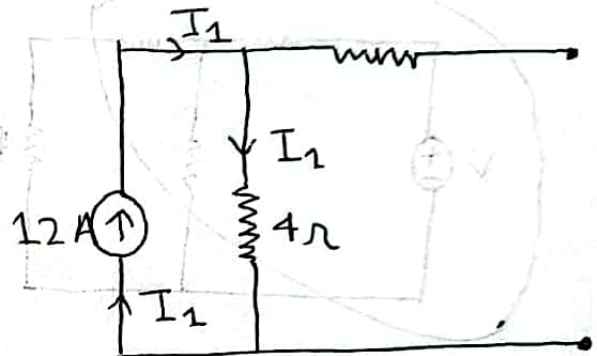

$$V_{TH} = I_1 R_1$$

$$= 12 \times 4$$

$$= 48V$$

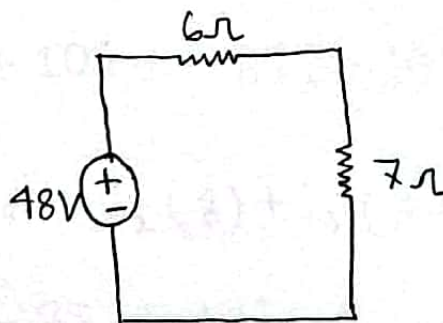


→ Thevenin's theorem

Ans:
2

Source transformation -


$$I = \frac{V}{R_{TH}}$$

$$= 8A$$

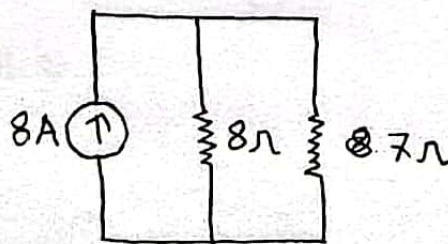

→ Norton's theorem

Source Transformation:

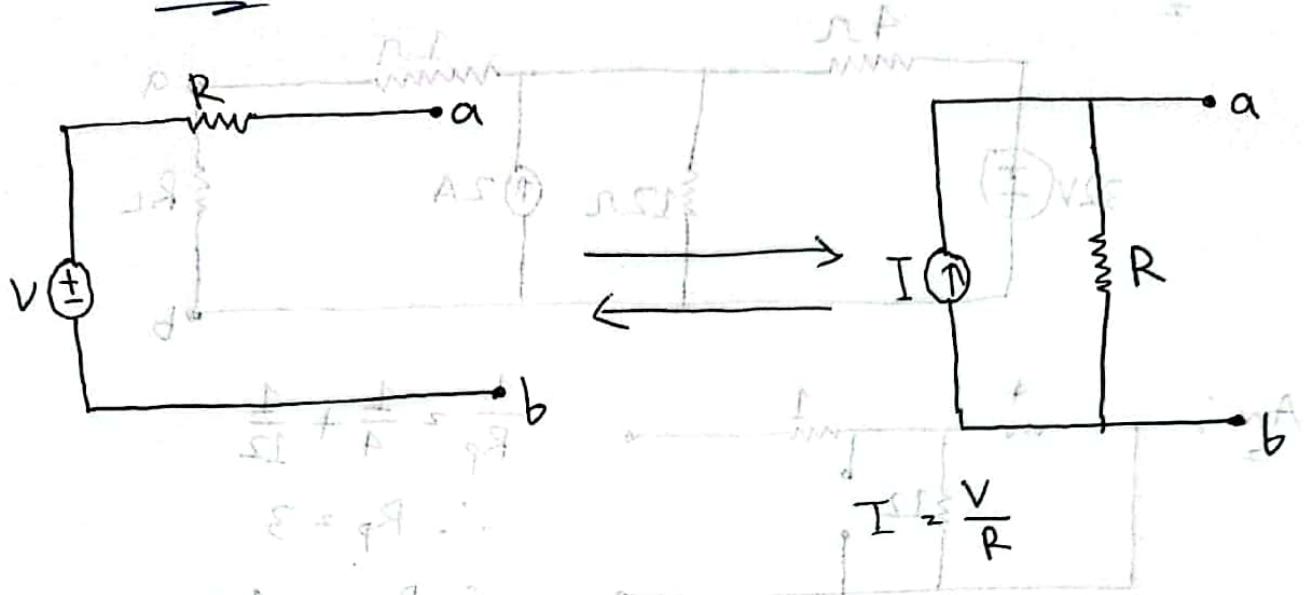


Voltage এর সাথে Resistor series এ থাকলে তাৎক্ষণিক source transformation করা যায়, কারণে current source এর resistor parallel এ হবে,



[V এর সাথে R Parallel এ হবে না]

$$\frac{0 - HTV}{\Delta I} = \Delta + \frac{HTV - \Delta \Delta}{\Delta} \quad (10)$$

$$VOS = HTV \quad \therefore$$

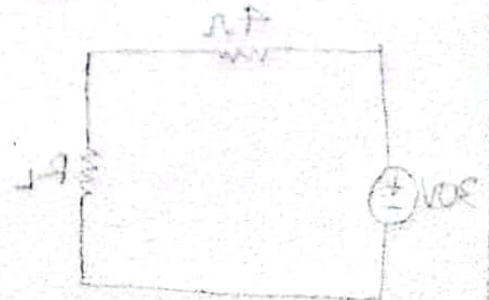



Ex-4.8

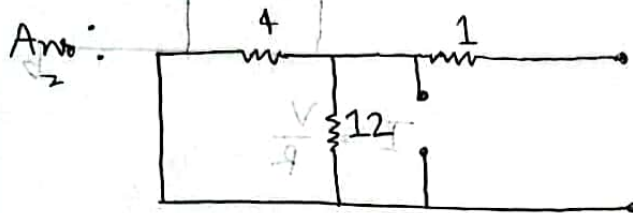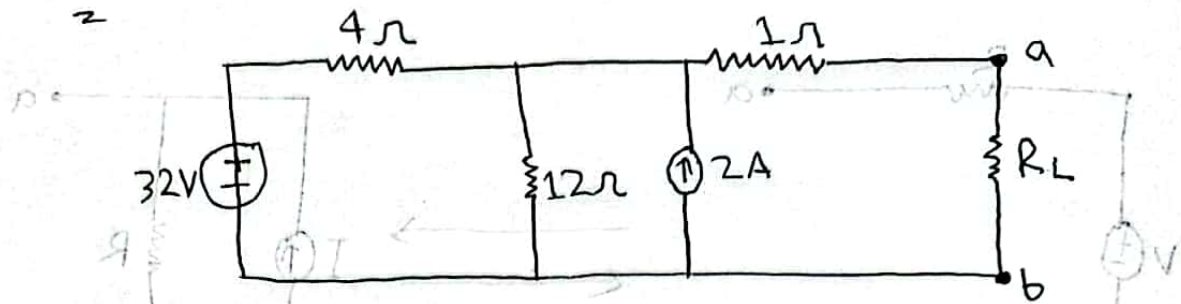

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{12}$$

$$\therefore R_p = 3$$

$$\therefore R_{TH} = 4\Omega$$

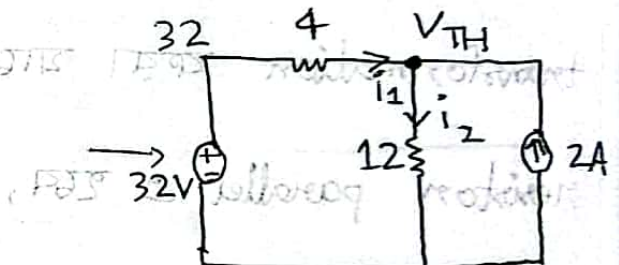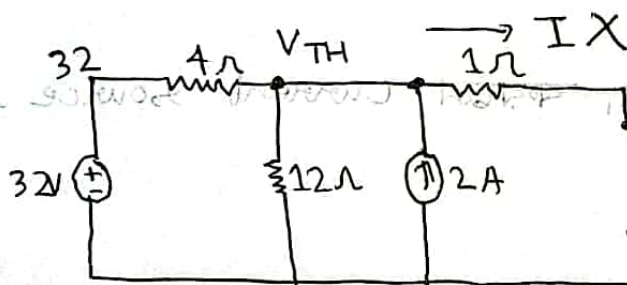

$$i_1 + 2 = i_2 \quad [\text{KCL at node } V_{TH}]$$

$$\text{or, } \frac{32 - V_{TH}}{4} + 2 = \frac{V_{TH} - 0}{12}$$

$$\therefore V_{TH} = 30V$$

Ans.

