

Segment 104

Signal and waveforms


(various units) Information

Signal: Signals are variables that carry information.

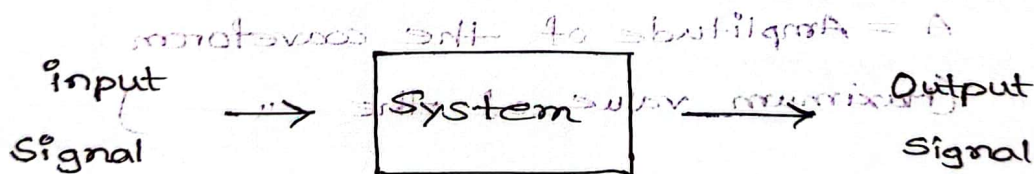Example: Audio, Video, Electrical signals (voltage & current)

System: System is an assemblage of entity/objects, real/abstract comprising a whole with each every component interacting with one another.

→ Process input signal to find output signal.



Example: Natural system


Human made system (computer programs, processor, machines,

Computer storage system etc)

Waveform: Shape of the signal is called waveform.

→ Sinusoidal (Sine, cosine)

→ Non-sinusoidal

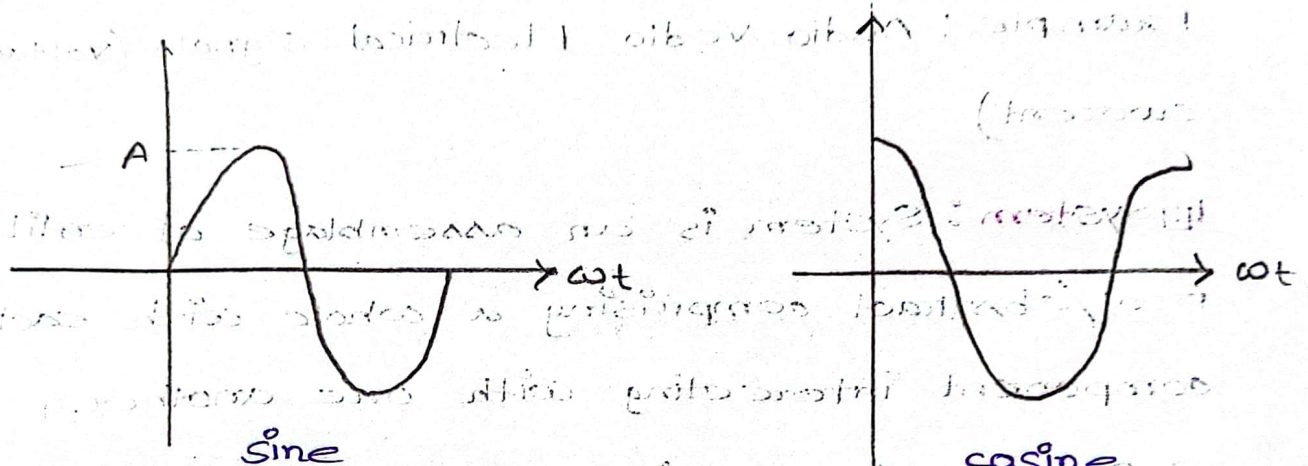


A = Amplitude of the waveform

(Maximum value of the waveform)


• Time period, $T = \frac{1}{f}$

* Non-Sinusoidal :-

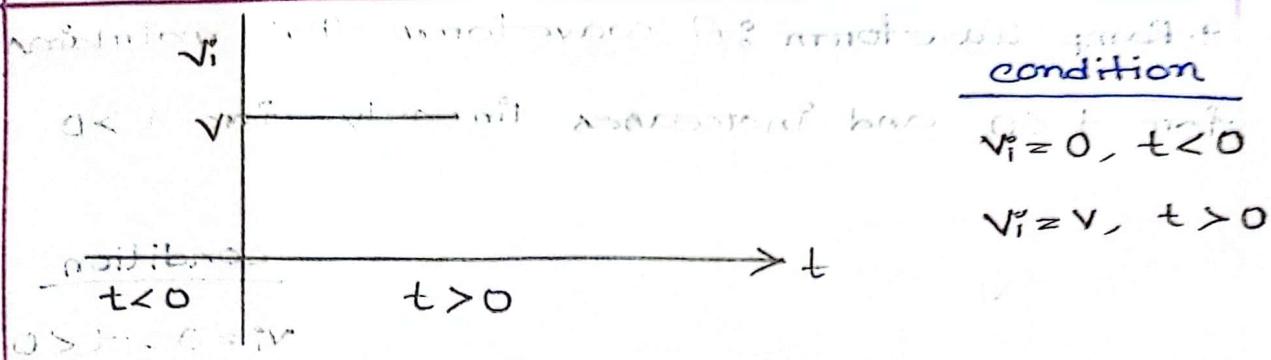
1. **Step waveform**: A waveform that maintains zero value for time $t < 0$ and maintains V for all the time $t > 0$.



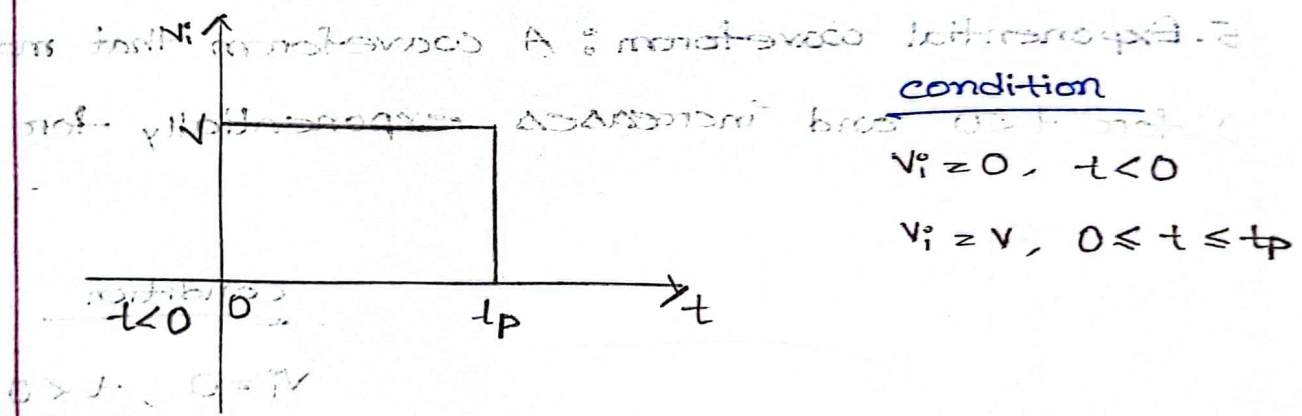
2. Pulse waveform : A waveform that maintains 0 for $t < 0$ and maintains V for time $t = 0$ to t_p , where t_p is the pulse duration.



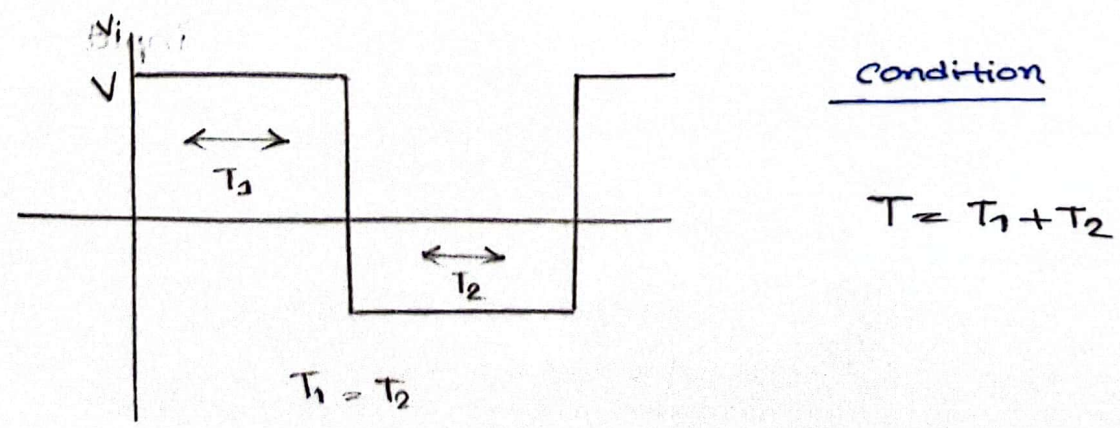3. Square waveform : A waveform that maintains one constant level for a time T_1 and another constant level for a time T_2 .



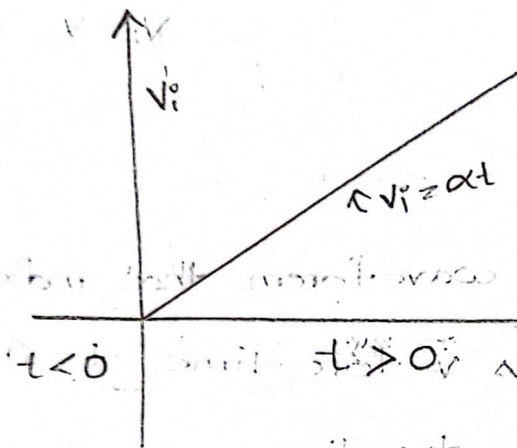4. Ramp Waveform : A waveform that maintains 0 for $t < 0$ and increases linearly for $t > 0$




condition

$$V_i = 0, t < 0$$

$$V_i = \alpha t, t > 0$$

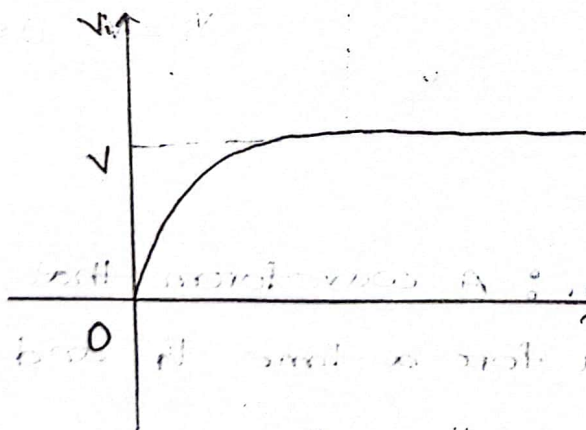5. Exponential waveform : A waveform that maintains 0 for $t < 0$ and increases exponentially for $t > 0$.



condition


$$V_i = 0, t < 0$$

$$V_i = V (1 - e^{-t/T}) t > 0$$

$T =$ time constant

of exponential input

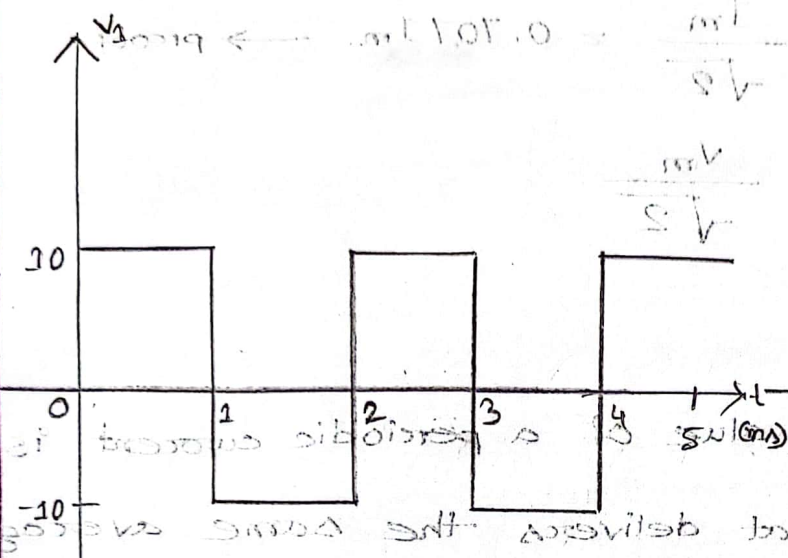Q Determine the average value of the waveforms:




$$V_1(\text{avg}) = \frac{\text{Amplitude} \times \text{Time duration}}{2} = \frac{(10 \times 1) + (-10 \times 1)}{2}$$

$$= 0V$$

$$V_2(\text{avg}) = \frac{(14 \times 1) + (-6 \times 1)}{2}$$

$$= 4V$$

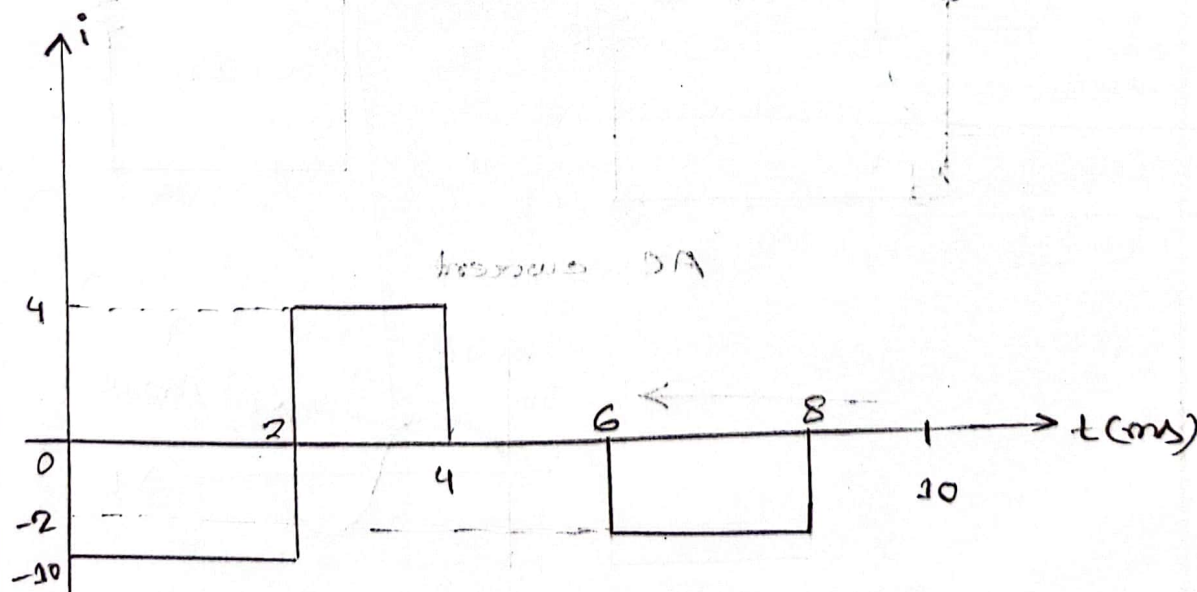

$$1 \text{ cycle } \Rightarrow T = 10 \text{ ms}$$

$$i(\text{avg}) = \frac{(-10 \times 2) + (4 \times 2) + (-2 \times 2)}{10} = -1.6V$$


Effective or RMS value

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = 0.707 I_m \rightarrow \text{proof}$$


$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

Proof :

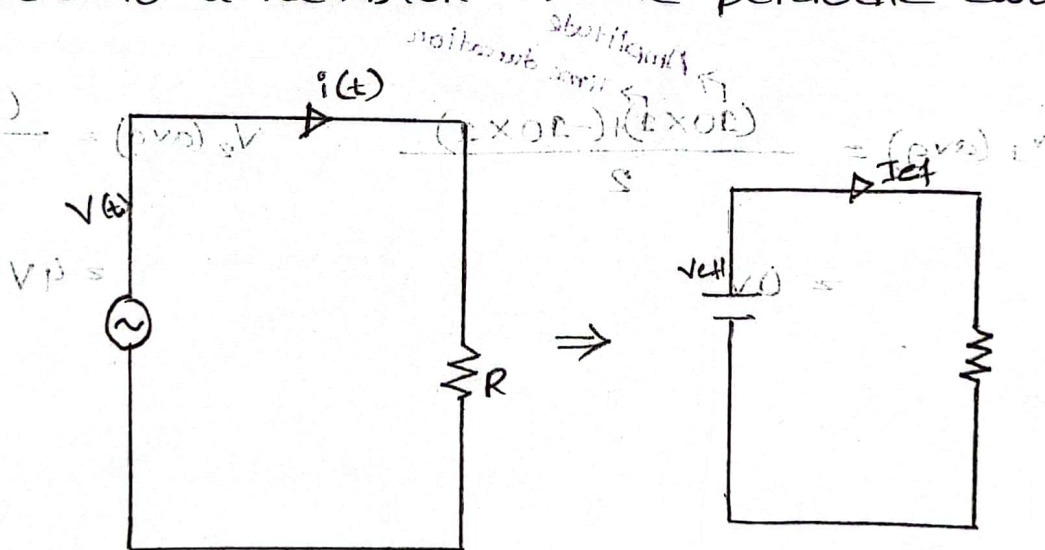The effective value of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current.



AC current

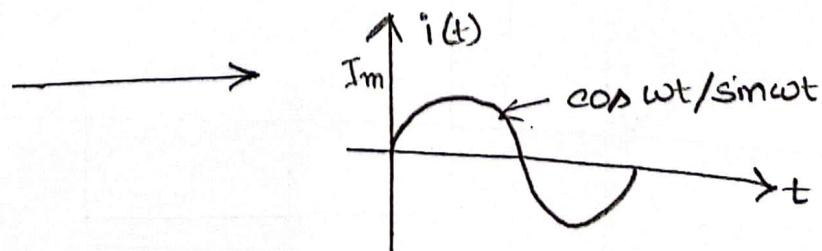

ANALYSIS OF AC CIRCUITS

$$(s \times s) + (s \times s) + (s \times s)$$

VOL

$$(s \times s) + (s \times s) + (s \times s)$$

For a sinusoid,

$$i(t) = I_m \cos \omega t$$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t dt}$$

$$= \sqrt{\frac{I_m^2}{2T} \int_0^T 2 \cos^2 \omega t dt}$$

$$= \sqrt{\frac{I_m^2}{2T} \int_0^T (1 + \cos 2\omega t) dt}$$

$$= \sqrt{\frac{I_m^2}{2T} \left[t \right]_0^T + \frac{I_m^2}{2T} \left[\frac{\sin 2\omega t}{2\omega} \right]_0^T}$$

$$= \sqrt{\frac{I_m^2}{2T} (T - 0) + \frac{I_m^2}{2T} \left[\frac{\sin 2 \cdot \frac{2\pi}{T} \cdot T}{2 \cdot \frac{2\pi}{T}} - \frac{\sin 2 \cdot \frac{2\pi}{T} \cdot 0}{2 \cdot \frac{2\pi}{T}} \right]}$$

$$= \sqrt{\frac{I_m^2}{2}}$$

$$\therefore I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

Same as V_{rms}

Proved


Segment - 5

Sinusoids and phasors

Sinusoid : A sinusoid is a signal that has the form of sine or cosine function.

→ General expression for sinusoid :

$$v(t) = V_m \sin(\omega t + \psi)$$

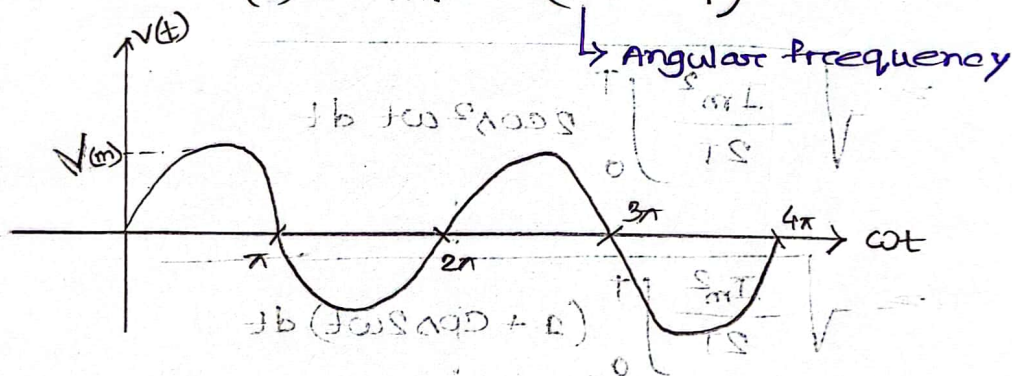

Q. * Given a sinusoid, $5 \sin(4\pi t - 60^\circ)$

Calculate :

amplitude = 5

phase = -60°

angular frequency = 4π

period = $\frac{1}{2}$ s

frequency = 2 Hz

$$f = \frac{4\pi}{2\pi}$$


$$\omega = 2\pi f$$

$$\therefore f = \frac{\omega}{2\pi}$$

$$T = \frac{1}{f}$$

$$= \frac{1}{2}$$


Ex phase of sinusoid (°) = ψ

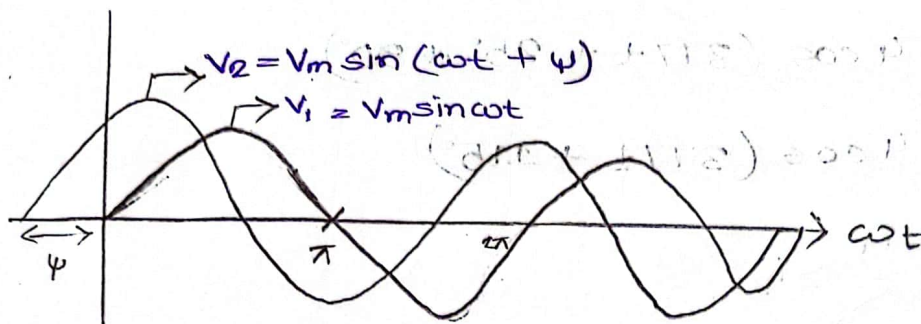

$\Rightarrow V_2$ leads V_1 by ψ :

$\Rightarrow V_1$ lags V_2 by ψ :

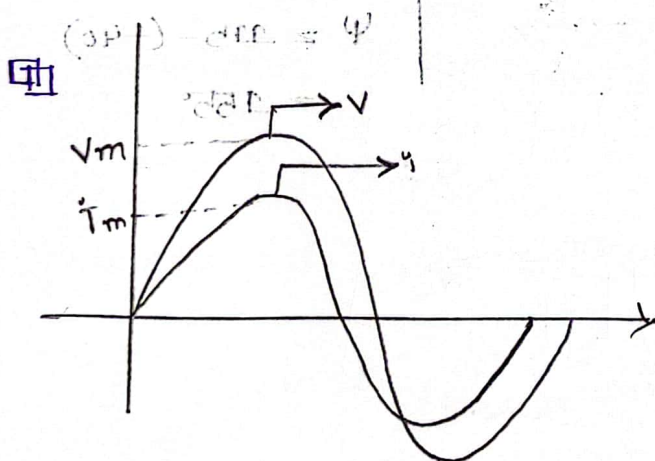* $\Rightarrow V_1$ and V_2 are out of phase



$\Rightarrow V$ and i are in-phase

Formula/Rules:

* $\sin(\omega t \pm 180^\circ) = -\sin \omega t$

($\cos + 180^\circ$) or ($\sin - 180^\circ$)

* $\cos(\omega t \pm 180^\circ) = -\cos \omega t$

($\sin + 180^\circ$) or ($\cos - 180^\circ$)

* $\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$

* $\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$

Q. * Find the phase angle between

$$i_1 = -4 \sin(377t + 25^\circ)$$


$$i_2 = 5 \cos(377t - 40^\circ)$$

does i_1 lead or lag i_2 ?

Ans : $i_1 = -4 \sin(377t + 25^\circ)$ because it is leading

$$= 4 \cos(377t + 25^\circ + 90^\circ)$$

$$= 4 \cos(377t + 115^\circ)$$

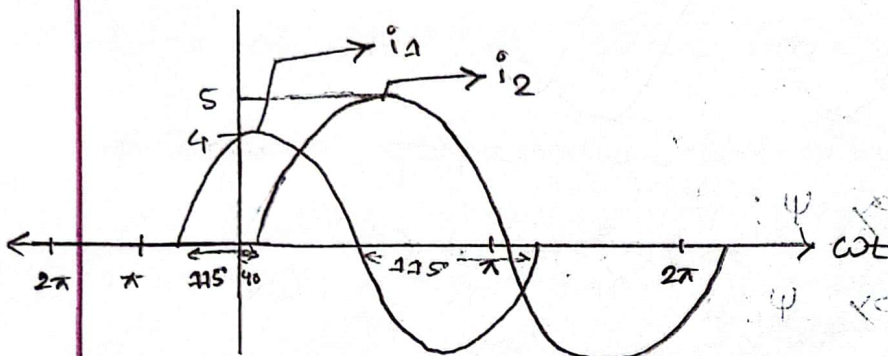

i_1 leads i_2 by 115°

phase difference

$$\psi = 115 - (-40)$$


$$= 155^\circ$$

Q * $v = 10 \sin(\omega t + 30^\circ)$

$i = 5 \sin(\omega t + 70^\circ)$

$i = 5 \sin(\omega t + 70^\circ)$

$v = 10 \sin(\omega t + 30^\circ)$

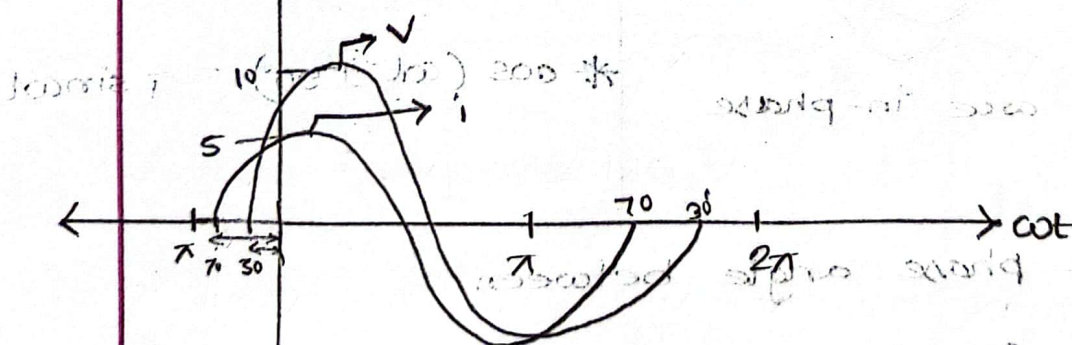


i leads v by $\psi = (70 - 30) = 40^\circ$

or,

v lags i by $\psi = 40^\circ$

Phasor (1)

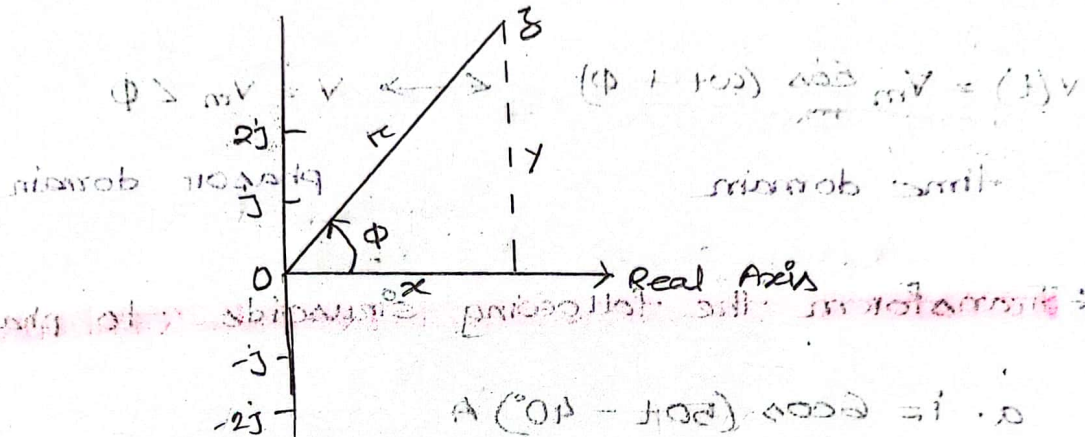A phasor is a complex number that represents the amplitude and phase of a sinusoid.



a. Rectangular : $z = x + jy = r(\cos \phi + j \sin \phi)$

b. Polar : $z = r \angle \phi$

c. Exponential : $z = r e^{j\phi}$

Phasor (2)

a. $[(5 + j2) (-1 + j4) - 5 \angle 60^\circ]$

using calculator $\rightarrow$

Ans : $-15.5 + 13.67j$

b. $\frac{10 + 5j + 3 \angle 40^\circ}{-3 + j4} + 10 \angle 30^\circ$

Ans : $8.293 + 2.2j$

Phasor (4) (1) 2020/09

- Transform a sinusoid to, and from the time domain to the phasor domain:

$$v(t) = V_m \cos(\omega t + \phi) \longleftrightarrow V = V_m \angle \phi$$

time domain

phasor domain

Q * Transform the following sinusoids to phasor:

a. $i = 6 \cos(50t - 40^\circ) \text{ A}$

b. $v = -4 \sin(30t + 50^\circ) \text{ V}$

Ans: a. $I = 6 \angle 40^\circ \text{ A}$

Ans: b. Since $-\sin A = \cos(A + 90^\circ)$:

$$v(t) = 4 \cos(30t + 50^\circ + 90^\circ)$$

$$= 4 \cos(30t + 140^\circ) \text{ V}$$

$$\therefore V = 4 \angle 140^\circ \text{ V}$$

Q * Transform the sinusoids corresponding to phasors:

a. $V = -10 \angle 30^\circ \text{ V}$

b. $I = j(5 - j12) \text{ A}$

Ans: a. $v(t) = 10 \cos(\omega t + 210^\circ) V$

Ans: b. Since,

$$I = 12 + j5$$

$$= \sqrt{12^2 + 5^2} \angle \tan^{-1}\left(\frac{5}{12}\right)$$

$$= 13 \angle 22.62^\circ$$

$$\therefore i(t) = 13 \cos(\omega t + 22.62^\circ) A$$

Q * a. $I = -3 + j4 A$

b. $V = j8e^{-j20} V$

Ans: a. $I = -3 + j4 A$

$$= \sqrt{(-3)^2 + (4)^2} \angle \tan^{-1}\left(-\frac{4}{3}\right) \rightarrow 5 \angle 126.9^\circ$$

$$= 5 \angle 126.9^\circ$$

$$\therefore i(t) = 5 \cos(\omega t + 126.9^\circ) A$$

Ans: b. Since $j = 1 \angle 90^\circ$

$$V = j8 \angle -20^\circ$$

$$= (1 \angle 90^\circ) (8 \angle -20^\circ)$$

$$= 8 \angle (90^\circ - 20^\circ) = 8 \angle 70^\circ V$$

$$\therefore v(t) = 8 \cos(\omega t + 70^\circ) \text{ V}$$

Phasor (8)

* Relationship between differential, integral, operation in phasor listed as follow:

$$v(t) \longleftrightarrow V = V \angle \phi$$

$$\frac{dv}{dt} \longleftrightarrow j\omega V$$

$$\int v dt \longleftrightarrow \frac{V}{j\omega}$$

$$V \cos \phi = V \cdot d$$

Q * Use phasor approach, determine the current $i(t)$ in a circuit described by the integro-differential equation. (Ans: $i(t) = 4.642 \cos(2t + 143.2^\circ) \text{ A}$)

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos\left(\frac{2t}{\omega t} + 75^\circ\right)$$

Ans:

$$4I + 8 \cdot \frac{I}{j\omega} - 3 \cdot j\omega I = 50 \angle 75^\circ$$

Phasor Relationships for circuit Elements (1)

• Resistor :


For $v = V_m \sin \omega t$

$$i = \frac{v}{R} = \frac{V_m \sin \omega t}{R}$$

$$= \frac{V_m}{R} \sin \omega t$$

$$i = I_m \sin \omega t$$

$$\bullet I_m = \frac{V_m}{R}$$

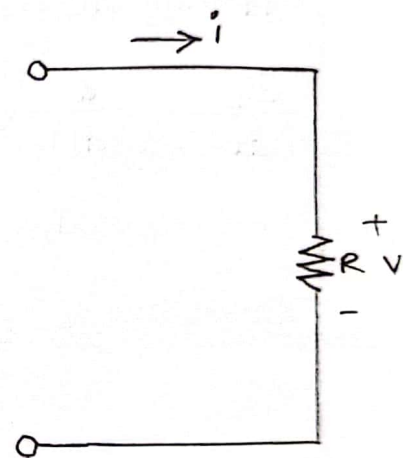


• in phase

For a given i ,

$$v = iR = (I_m \sin \omega t) R$$

$$= V_m \sin \omega t$$

$$\bullet V_m = I_m R$$

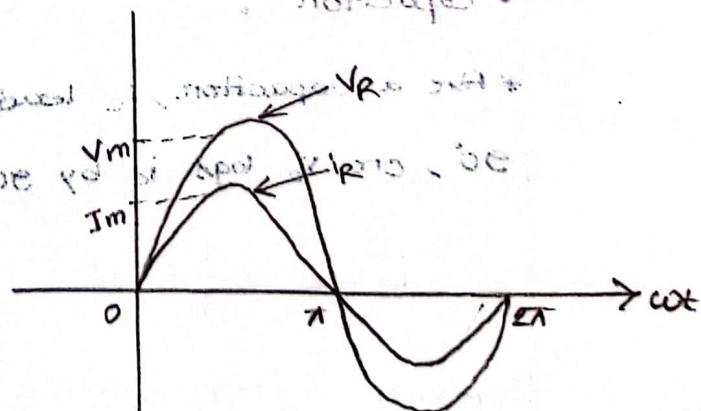

• Inductor :

* An inductor V_L leads i_L by 90°

or, i_L lags V_L by 90° .

$$V_L = L \frac{di_L}{dt}$$

Applying differentiation,

$$\frac{di_L}{dt} = \frac{d}{dt} (I_m \sin \omega t)$$

$$= \omega I_m \cos \omega t$$

Therefore, $V_L = L \frac{di_L}{dt}$

$$= L (\omega I_m \cos \omega t)$$

$$= \omega L I_m \cos \omega t$$

or,

$$V_L = V_m \sin(\omega t + 90^\circ)$$

$$* V_m = \omega L I_m$$

$$\frac{V_m}{I_m} = \omega L$$

• Capacitor :

* For a capacitor, i_C leads V_C by



90° , or V_C lags i_C by 90°

$$i_C = C \frac{dV_C}{dt}$$

Applying differentiation,

$$\frac{dV_C}{dt} = \frac{d}{dt} (V_m \sin \omega t)$$

$$= \omega V_m \cos \omega t$$

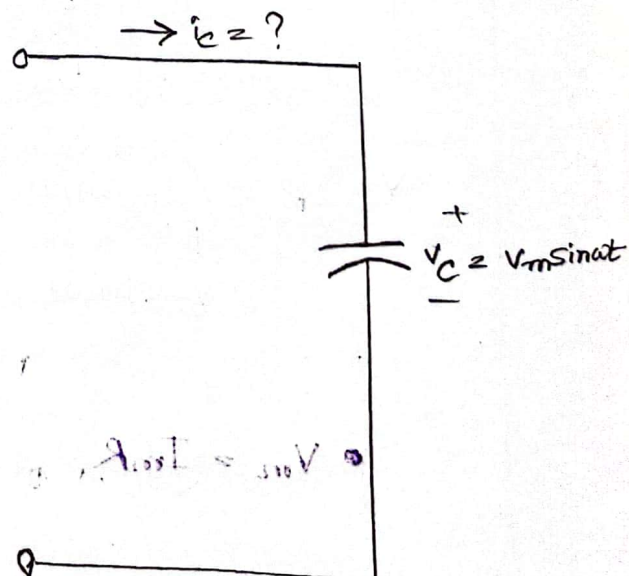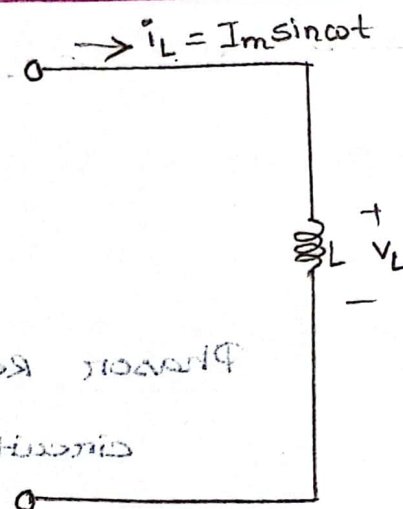

Therefore, $i_c = C \frac{dv_c}{dt}$

$$= C (\omega V_m \cos \omega t)$$

$$= \omega C V_m \cos \omega t$$

$$\text{OR, } i_c = I_m \sin(\omega t + 90^\circ)$$


$$\therefore I_m = \omega C V_m$$

$$* X_c = \frac{V_m}{I_m} = \frac{V_m}{\omega C V_m} = \frac{1}{\omega C}$$

Capacitor এর Capacitance or, reactance

● Circuit :


* Resistor এর জন্য phasor Diagram:

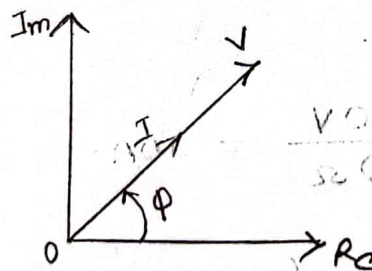

Voltage এর, current এর
মধ্যে difference নাই, $\phi = 0$


In-phase
তাই যেখানে যেখানে I, সেখানেই V,

* Inductor এর জন্য phasor Diagram:

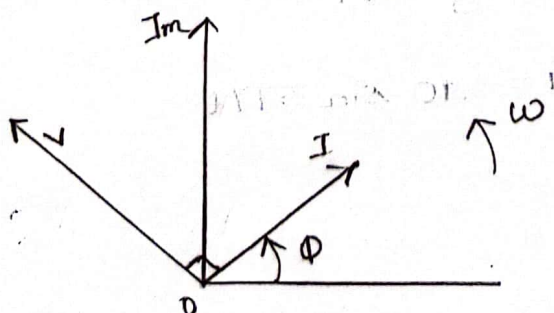

V, I কে 90° এ lead করে

* Capacitors and phasor Diagram:

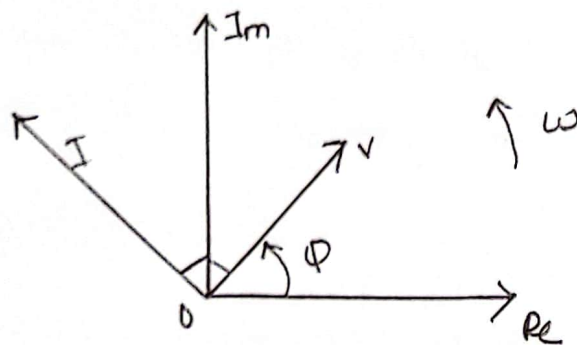

I, V are lead/lag,

$$\sin(\omega t) = \cos(\omega t - 90^\circ)$$

Q * Example: 14.11 The voltage across a resistor is indicated. Find the sinusoidal expression for the current if the resistor is 10Ω . Sketch the waves for v and i .

a. $V = 100 \sin 377t$


b. $V = 25 \sin(377t + 60^\circ)$

$\Rightarrow$ We know,

Ans: a
$$I_m = \frac{V_m}{R} = \frac{100V}{10\Omega} = 10A$$

It's a resistor, so that (v and i are in-phase) resulting in,

$$i = 10 \sin 377t$$

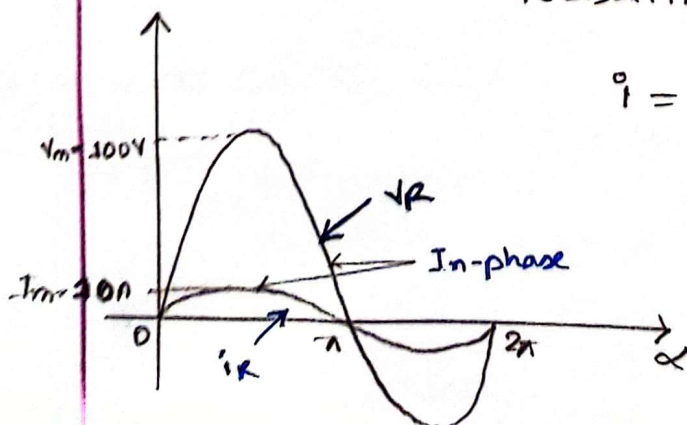


∴ we know, $V = IR$

Ans: b.

$$I_m = \frac{V_m}{R} = \frac{25V}{10\Omega} = 2.5A$$

It's a resistor, so that V and I are in-phase

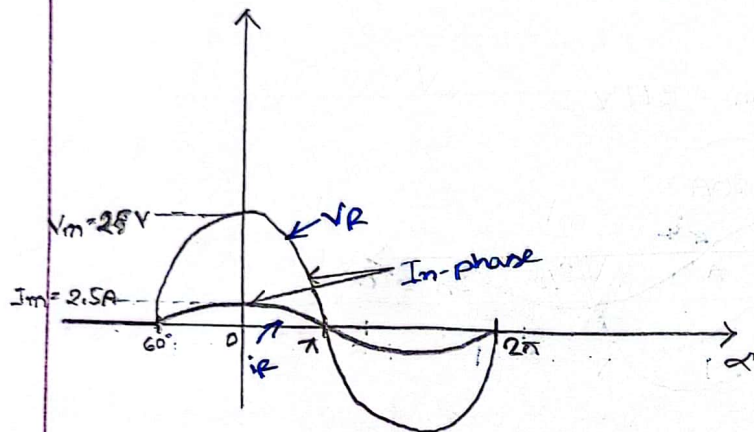resulting in, $i = 2.5 \sin(377t + 60^\circ)$



Q * Example: 14.3 | The current through a 0.1-H coil/inductor is provided. Find the sinusoidal expression for the voltage across the coil. Sketch the V and i curves.

a. $i = 10 \sin 377t$

b. $i = 7 \sin(377t - 70^\circ)$

∴ we know,

Ans: a. $X_L = \omega L$

$$X_L = (377 \text{ rad/s})(0.1H)$$

$$X_L = 37.7\Omega$$

$$V_m = I_m X_L = (10A)(37.7\Omega) = 377V$$


এখানে, X_L হল ইন্ডাকটিভ রিসিস্ট্যান্স।
 * X_L হল ইন্ডাকটিভ রিসিস্ট্যান্স।
 * Resistance, এখানে Inductance
 এবং X_L হল ইন্ডাকটিভ ইন্ডাক্ট্যান্স
 * Ohm's Law, $V_m = I_m X_L$
 ∴ Inductor - এর জন্য, হবে,
 $V_m = I_m X_L$

Also we know that for a coil/inductor v leads i by

90° , therefore,

$$v = 377 \sin(377t + 90^\circ)$$

The curves are sketched,

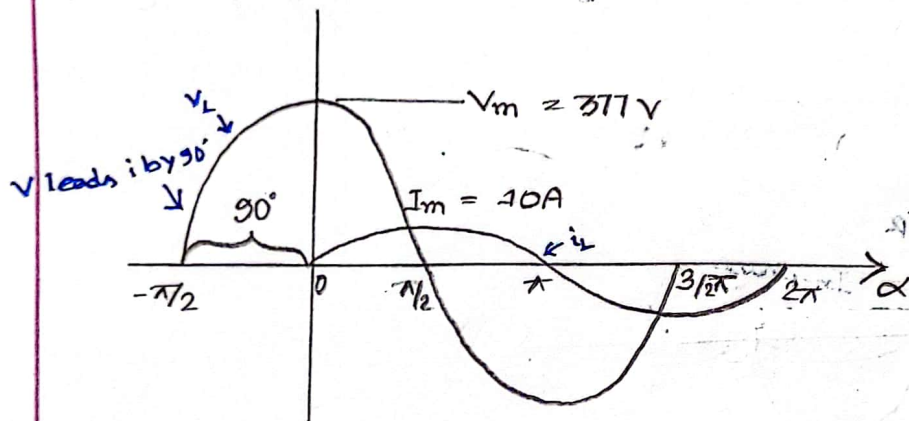

⇒ from 'a' we got,

Ans: b.

X_L remains at 37.7Ω

And, $V_m = I_m X_L$

$$= (7A)(37.7 \Omega)$$

$$= 263.9 V$$


also we know that for a coil/inductor v leads i

by 90° , therefore,

$$v = 263.9 \sin(377t - 70^\circ + 90^\circ)$$

$$\text{or, } v = 263.9 \sin(377t + 20^\circ)$$

The curves are sketched,

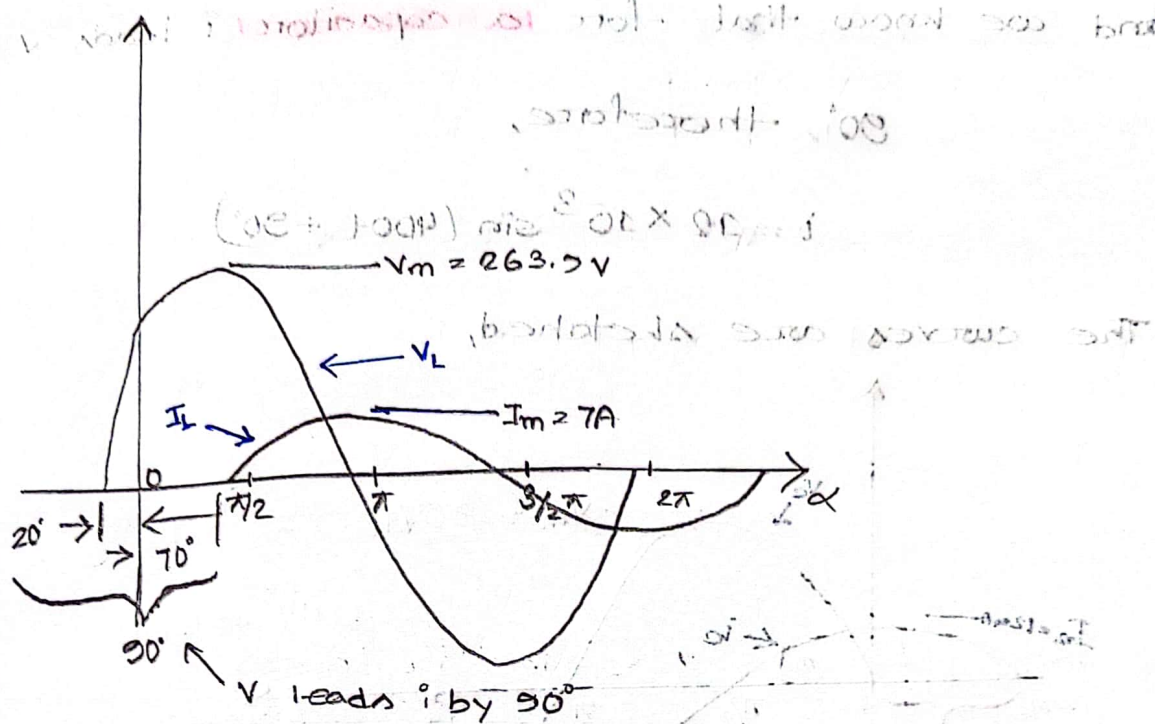

Q * Example 14.51 The voltage across a $1 \mu\text{F}$ capacitor is provided below. what is the sinusoidal expression for the current? Sketch the v and i waves.

Given $v = 30 \sin 400t$

We know, $X_C = \frac{1}{\omega C} = \frac{1}{(400 \text{ rad/s}) (1 \times 10^{-6} \text{ F})}$

Capacitor - $\Rightarrow$ Capacitance $= 2500 \Omega$

Again, $I_m = \frac{V_m}{X_C} = \frac{30}{2500}$


$I_m = 0.012 \text{ A}$

$I_m = 12 \text{ mA}$

and we know that for a capacitor i leads v by 90° , therefore,

$$i = 12 \times 10^{-3} \sin(400t + 90^\circ)$$


The curves are sketched,

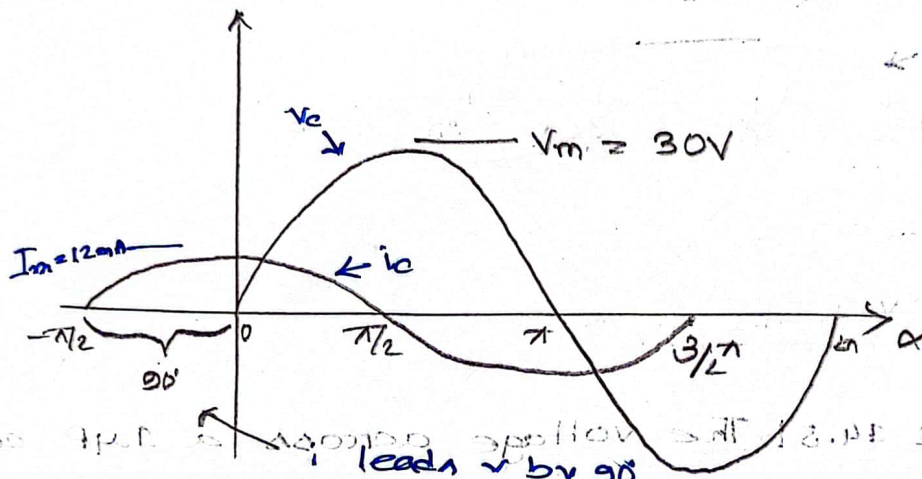

* Example: 14.7/ For the following pairs of voltages and currents, determine whether the element involved is a capacitor, an inductor, or a resistor and determine the value of C , L , or R if sufficient data are provided.

a. $v = 100 \sin(\omega t + 40^\circ)$

$i = 20 \sin(\omega t + 40^\circ)$

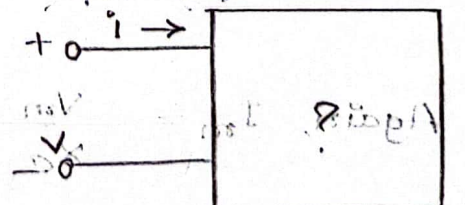

$\Rightarrow$ phase difference, $\psi = 40 - 40$

$= 0^\circ$, in-phase

so that, it's a resistor.

Given, $V_m = 100 \text{ V}$ $R = \frac{V_m}{I_m} = \frac{100}{20}$

$I_m = 20 \text{ A}$

$= 5 \Omega$

b. $v = 1000 \sin(377t + 10^\circ)$

$i = 5 \sin(377t - 80^\circ)$

$\Rightarrow$ phase difference, $\phi = 10 + 80$

$= 90^\circ$

it's an inductor, cause v leads i by 90°

Given, $V_m = 1000 \text{ V}$

$I_m = 5 \text{ A}$

$L = \frac{V_m}{I_m \omega}$

$= \frac{1000}{5 \times 377}$

$= 0.53 \text{ H}$

c. $v = 500 \sin(157t + 30^\circ)$

$i = 1 \sin(157t + 120^\circ)$

$\Rightarrow$ phase difference, $\phi = 120 - 30$

$= 90^\circ$

It's a capacitor, cause i leads v by 90°

Given, $I_m = 1A$

$$V_m = 500V$$

$$\omega = 157$$

$$\therefore C = \frac{I_m}{V_m \omega}$$

(or) $C = \frac{1}{\omega Z}$ (or) $C = \frac{1}{\omega R}$

$$= \frac{1}{157 \times 500}$$

$$= 12.738 \times 10^{-6} F$$

$$= 0.0127 \mu F$$

$$v = 50 \cos(\omega t + 20^\circ)$$

$$i = 5 \sin(\omega t + 110^\circ)$$

$$\Rightarrow i = 5 \cos(\omega t + 110 - 90)$$

$$= 5 \cos(\omega t + 20^\circ)$$

$\therefore$ phase difference, $\phi = 20 - 20$

$$= 0 \therefore \text{in-phase}$$

So that it's a resistor

Given, $V_m = 50V$

$$I_m = 5A$$

$$\therefore R = \frac{V_m}{I_m} = \frac{50V}{5A}$$

$$= 10\Omega$$

Phasor Relationships for Circuit Elements

Example: If voltage $v(t) = 6 \cos(100t - 30^\circ)$ is applied to a $50 \mu\text{F}$ capacitor, calculate the current, $i(t)$, through the capacitor.

$$\Rightarrow v(t) = 6 \cos(100t - 30^\circ)$$

$$\text{We know, } X_C = \frac{1}{\omega C} = \frac{1}{(100 \text{ rad/s})(50 \times 10^{-6})}$$

$$= 200 \Omega$$

$$\text{Again, } I_m = \frac{V_m}{X_C}$$

$$= \frac{6}{200} = 30 \text{ mA}$$

And, we know that for a capacitor i leads v by 90° , therefore,

$$i(t) = 30 \sin(100t - 30^\circ + 90^\circ)$$

$$= 30 \cos(100t + 60^\circ) \text{ mA}$$

Impedance and Admittance

$$* Z = \frac{V}{I} = R + jX$$

It's Impedance, Unit Ω .

where $R = \text{Re}$, Z is the resistance and $X = \text{Im}$,
 Z is the reactance. Positive X is for L and
 negative X is for C .



* The admittance Y is the reciprocal of impedance,
 measured in siemens (S).

$$\square Y = \frac{1}{Z} = \frac{I}{V}$$



Impedances and admittances of passive elements

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

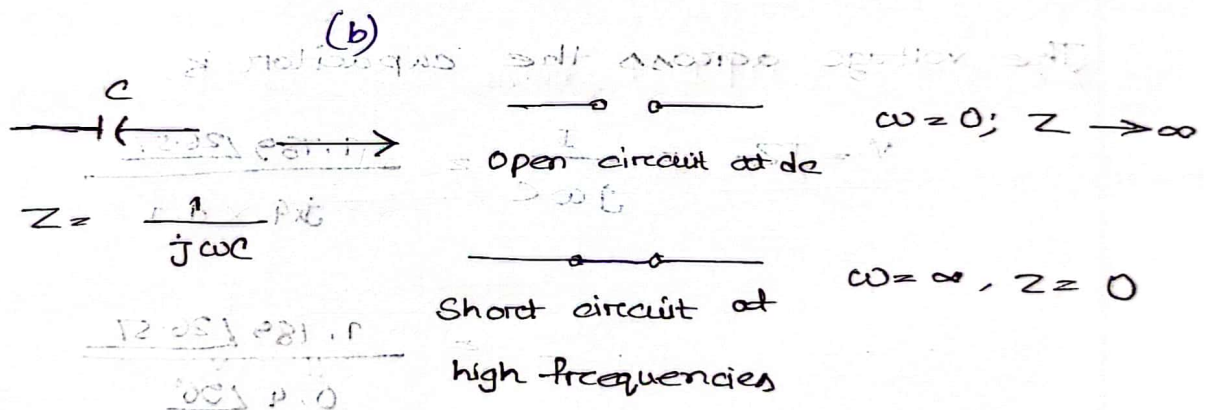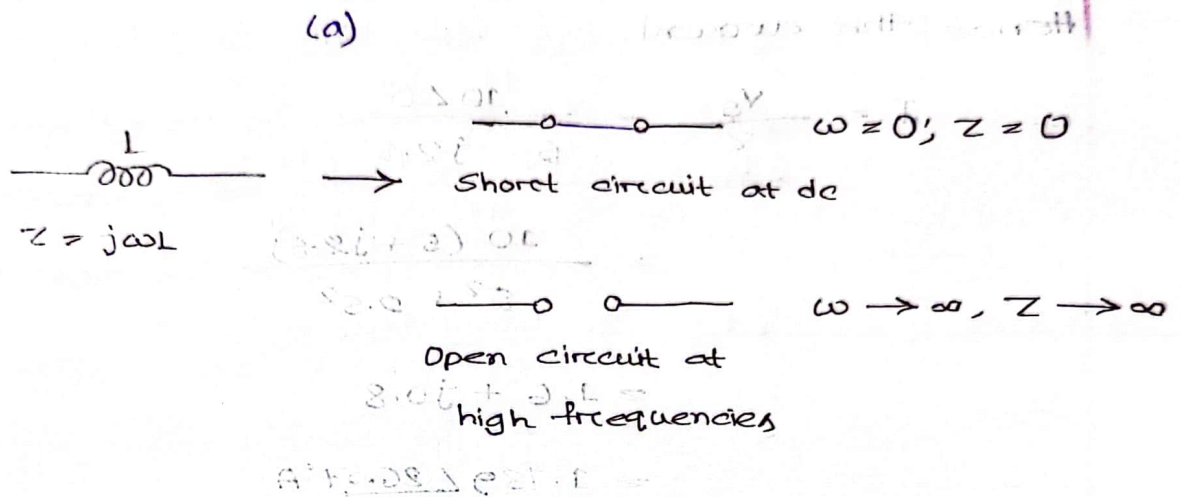

Q * Example: 9.9. Find $v(t)$ and $i(t)$ in the circuit.


From the voltage source $10 \cos 4t$,

$\omega = 4$, $V_s = 10 \angle 0^\circ \text{ V}$

$V_s = 10 \angle 0^\circ \text{ V}$

The impedance is

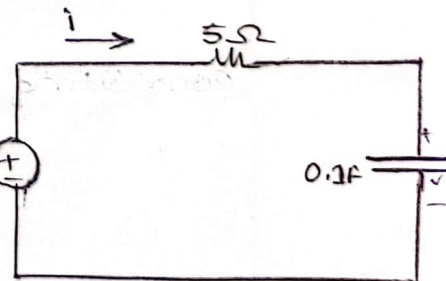$Z = 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j \times 4 \times 0.1} = 5 - j2.5 \Omega$



Hence the current,

$$\begin{aligned}
 I &= \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{5 - j2.5} \\
 &= \frac{10 (5 + j2.5)}{5^2 + 2.5^2} \\
 &= 1.6 + j0.8 \\
 &= 1.789 \angle 26.57^\circ \text{ A}
 \end{aligned}$$

The voltage across the capacitor is,

$$\begin{aligned}
 V &= I Z_C = \frac{I}{j\omega C} = \frac{1.789 \angle 26.57^\circ}{j4 \times 0.1} \\
 &= \frac{1.789 \angle 26.57^\circ}{0.4 \angle 90^\circ}
 \end{aligned}$$

$$= 4.47 \angle -63.43^\circ \text{ V}$$

Converting I and V to the time domain we get,

$$i(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$

$$v(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$


Notice that $i(t)$ leads $v(t)$ by 90° as expected.

Example: 9.10. Find the input

impedance of the circuit.

Assume that the circuit operates

at $\omega = 50 \text{ rad/s}$.

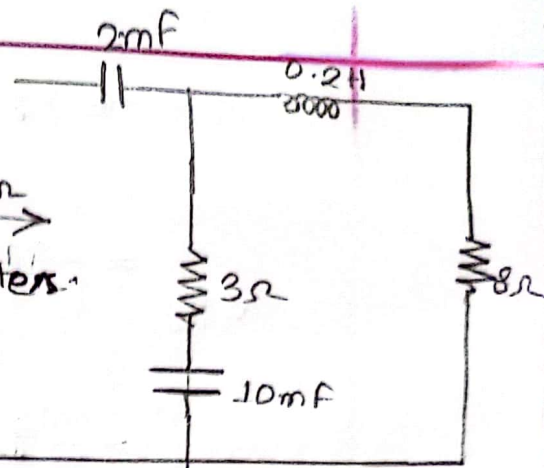

⇒ Let,

Z_1 = Impedance of the 2mF capacitor

Z_2 = Impedance of the 3Ω resistor in series with the 10mF capacitor.

Z_3 = Impedance of the 0.2H inductor in series with the 8Ω resistor.

Then

$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j \times 50 \times 2 \times 10^{-3}} = -j10\Omega$$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j \times 50 \times 10 \times 10^{-3}} = (3 - j2)\Omega$$

$$Z_3 = 8 + j\omega L = 8 + j \times 50 \times 0.2$$

$$= (8 + j10)\Omega$$

The input impedance is

$$Z_{in} = Z_1 + Z_2 \parallel Z_3$$

$$= -j10 + \frac{(3-j2)(8+j10)}{11+j8}$$


$$= -j10 + \frac{(44 + j14)(11-j8)}{11^2 + 8^2}$$

$$= -j10 + 3.22 - j1.07 \Omega$$

Thus,

$$Z_{in} = 3.22 - j1.07 \Omega$$

Q * Example: 9.11 | Determine $v_o(t)$ in the circuit.

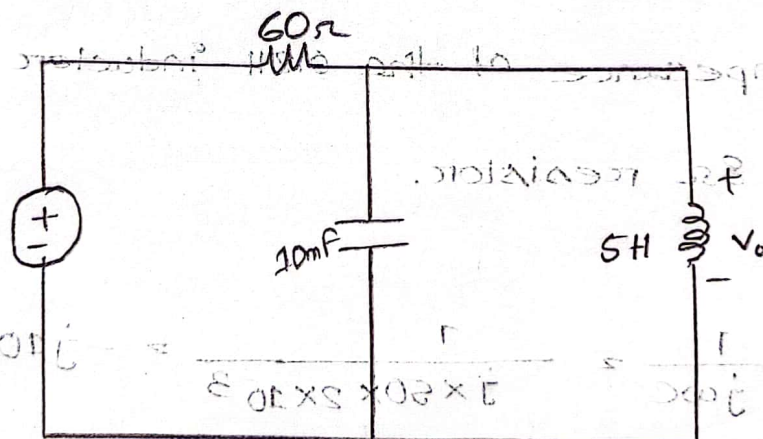


To do the analysis in the frequency domain, we must first transform the time domain circuit to the phasor domain equivalent.

The transform produces,

$$V_s = 20 \angle -15^\circ \text{ V}, \omega = 4$$

$$10 \text{ mF} \Rightarrow \frac{1}{j\omega C} = \frac{1}{j \times 4 \times 10 \times 10^{-3}}$$

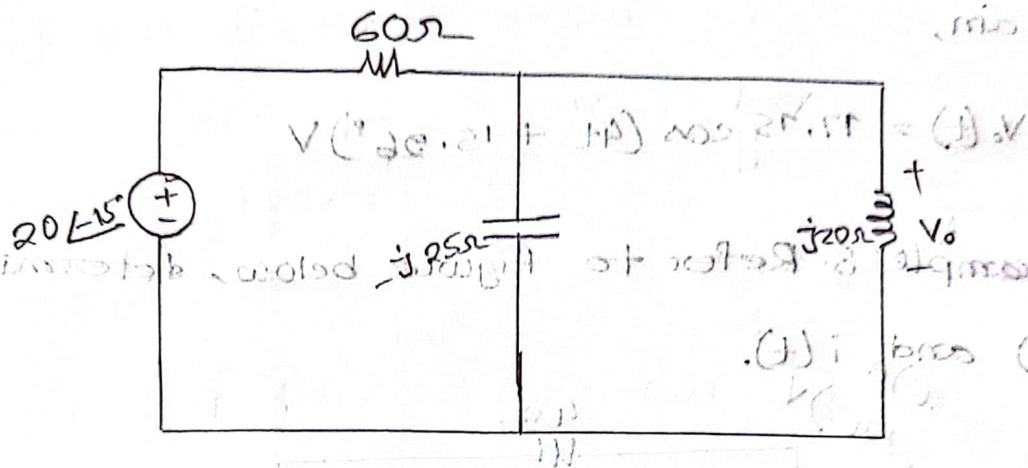Inductive reactance $\Rightarrow j\omega L = j \times 4 \times 5 = j20\Omega$



Let,

Z_1 = Impedance of the 60Ω resistor

Z_2 = Impedance of the parallel combination of the 10mF capacitor and the 5H inductor

Then $Z_1 = 60\Omega$ and

$$Z_2 = -j25 \parallel j20 = \frac{-j25 \times j20}{-j25 + j20}$$

$$= j100\Omega$$

By the voltage division principle,

$$V_0 = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{j100}{60 + j100} (20\angle -15^\circ)$$

$$= (0.8575 \angle 30.96^\circ) (20\angle -15^\circ)$$

$$= 17.15 \angle 15.96^\circ \text{ V}$$

We convert this to the time domain and obtain,

$$V_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V}$$

§ * Example: 8. Refer to figure below, determine


$v(t)$ and $i(t)$.

Ans:


$$i(t) = 1.118 \cos(10t - 26.56^\circ) \text{ A}$$

$$v(t) = 2.236 \cos(10t + 63.43^\circ) \text{ V}$$

$$V_s = 5 \cos(10t) \text{ V}$$

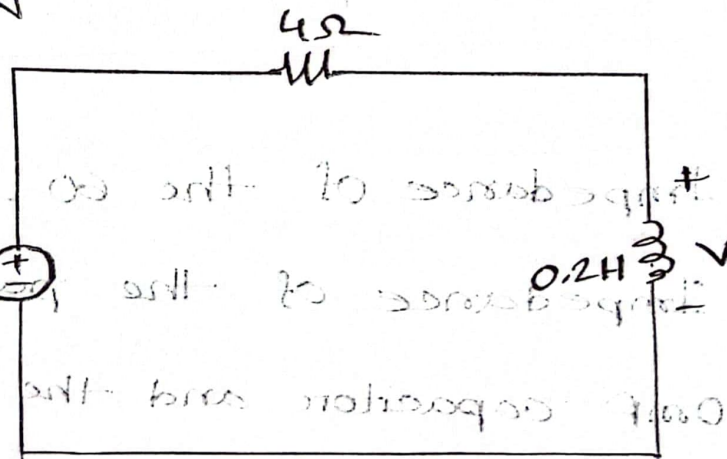

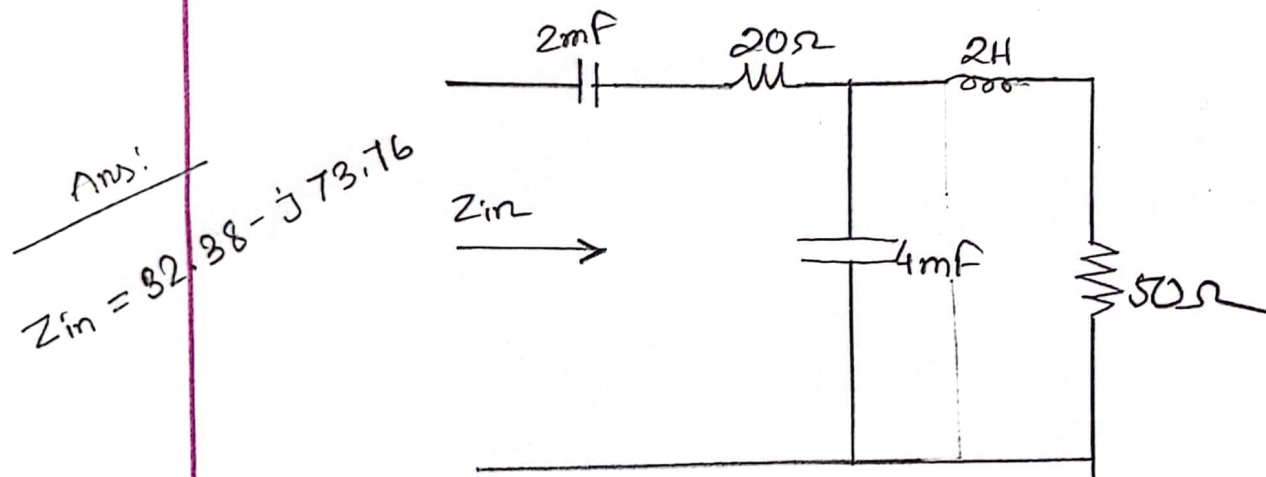Q. Example: 9. Determine the input impedance of the circuit in figure below at $\omega = 10 \text{ rad/s}$



Let,

$Z_1 =$ Impedance of the 2-mF capacitor

$Z_2 =$