

Concepts of current: If dq is the amount of net charge that passes through any surface in a time interval dt , then the current ' i ' is given by,


$$i = \frac{dq}{dt}$$

If the rate of flow of charge is constant in time, the current is said to be steady ~~or~~ constant. Denoting the constant current by ' I ' we simply get,

$$I = \frac{q}{t}$$

where q is the total ^{charge} ~~current~~ flow ~~of~~ in time t .

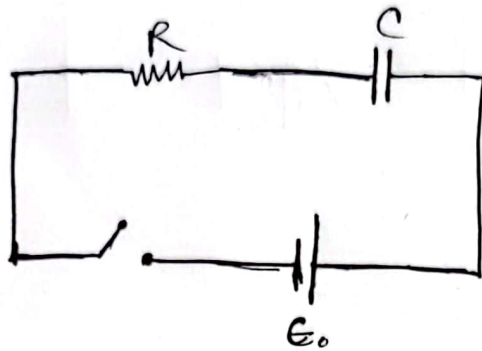RC Circuit: The circuit which ~~is~~ is consist of Resistor & Capacitor is called R-C circuit.



Conditions—

- i) Growth of a charge in capacitor (charging).
- ii) Decay of a charge in capacitor (discharging)


Growth of a charge:

The potential difference ~~across~~ across the Resistor,

$$V = RI$$

And the potential difference across the Capacitor,

$$V = \frac{q}{C}$$

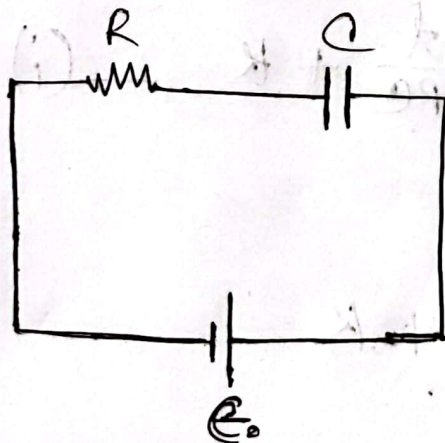

According to KVL,

$$\mathcal{E}_0 = RI + \frac{q}{C}$$

$$\Rightarrow \mathcal{E}_0 = R \cdot \frac{dq}{dt} + \frac{q}{C}$$

$$\Rightarrow \mathcal{E}_0 - \frac{q}{C} = R \cdot \frac{dq}{dt}$$

$$\Rightarrow \frac{\mathcal{E}_0 C - q}{C} = R \cdot \frac{dq}{dt}$$

$$\Rightarrow \frac{C}{\mathcal{E}_0 C - q} = \frac{dt}{R \cdot dq}$$

$$\Rightarrow \frac{dq}{\mathcal{E}_0 C - q} = \frac{dt}{RC}$$

$$\Rightarrow \frac{dq}{q - \mathcal{E}_0 C} = - \frac{dt}{RC}$$



$$\Rightarrow \int \frac{dq}{q - \mathcal{E}_0 C} = - \int \frac{dt}{RC}$$

$$\Rightarrow \ln|q - \mathcal{E}_0 C| = - \frac{t}{RC} + K \quad (i)$$

when $t = 0$, then $q = 0$,

$$\ln|0 - \mathcal{E}_0 C| = -0 + K$$

$$\therefore K = \ln|-\mathcal{E}_0 C|$$

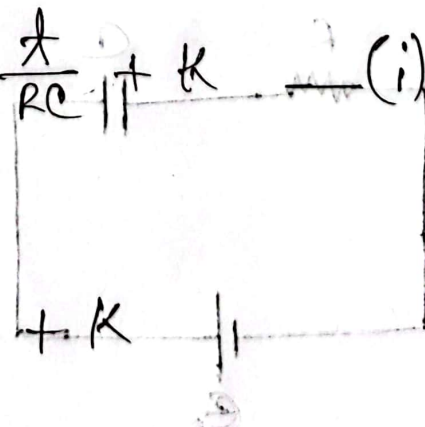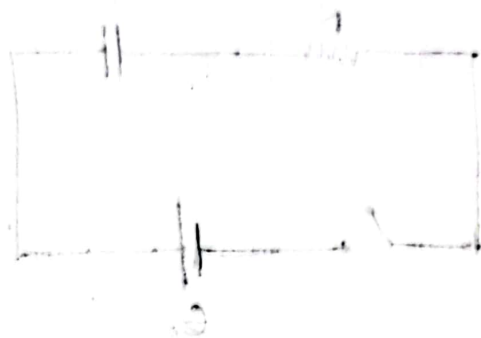

placing value of K in eqn (i),

$$\ln |q - ce_0| = -\frac{t}{RC} + \ln (-ce_0)$$


$$\Rightarrow \ln \left| \frac{q - ce_0}{-ce_0} \right| = -\frac{t}{RC}$$

$$\Rightarrow -\frac{q}{ce_0} + 1 = e^{-t/RC}$$

$$\Rightarrow \frac{q}{ce_0} - 1 = -e^{-t/RC}$$

$$\Rightarrow \frac{q}{ce_0} = 1 - e^{-t/RC}$$

$$\therefore q = ce_0 (1 - e^{-t/RC})$$

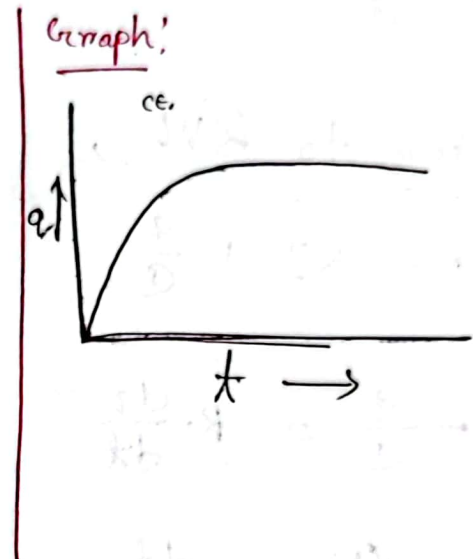

For maximum charge, $q_0 = ce_0$

we know,

$$I = \frac{dq}{dt}$$


$$= \frac{d}{dt} \{ ce_0 (1 - e^{-t/RC}) \}$$

$$= ce_0 \cdot \frac{d}{dt} (1 - e^{-t/RC})$$

$$= ce_0 \cdot (0 + e^{-t/RC} \cdot \frac{1}{RC})$$

$$= ce_0 \cdot \frac{1}{RC} \cdot e^{-t/RC}$$
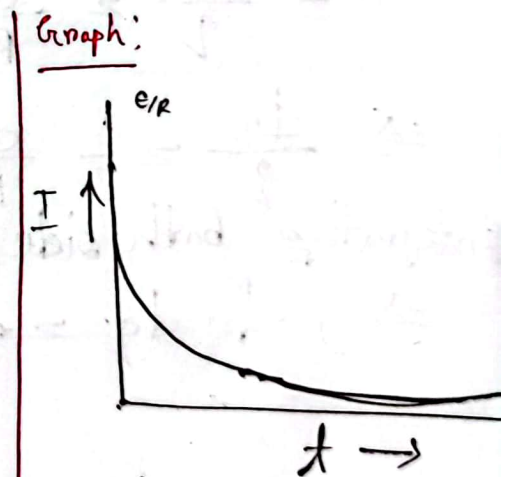
$$\therefore I = \frac{e_0}{R} \cdot e^{-t/RC}$$




Decay of charge:

Again,

$$V_R = RI$$

$$\text{and, } V_C = \frac{q}{C}$$

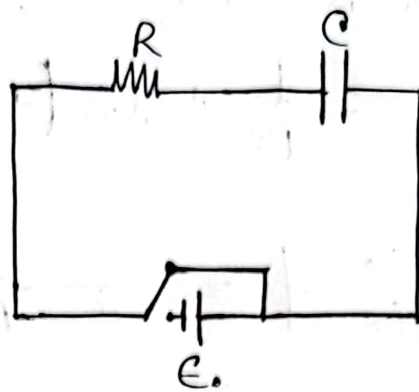

According to KVL,

$$0 = RI + \frac{q}{C}$$

$$\Rightarrow -\frac{q}{C} = R \cdot \frac{dq}{dt}$$

$$\Rightarrow -\frac{C}{q} = \frac{dt}{R \cdot dq}$$

$$\Rightarrow -\frac{dq}{q} = \frac{dt}{RC}$$

$$\Rightarrow \frac{dq}{q} = -\frac{dt}{RC}$$

Integrating both side,

$$\Rightarrow \int \frac{1}{q} dq = \int \frac{-1}{RC} dt$$

$$\Rightarrow \ln(q) = -\frac{t}{RC} + K \quad \text{--- (i)}$$

when, $t = 0$, then, $q = q_0 = C\mathcal{E}_0$

$$\Rightarrow \ln(q_0) = \cancel{0} + K$$

$$\therefore K = \ln(C\mathcal{E}_0)$$

placing the value of K in eqn (i),


$$\ln|q| = -\frac{t}{RC} + \ln|ce_0|$$

$$\Rightarrow \ln|q| - \ln|ce_0| = -\frac{t}{RC}$$

$$\Rightarrow \ln\left|\frac{q}{ce_0}\right| = -\frac{t}{RC}$$

$$\Rightarrow \frac{q}{ce_0} = e^{-t/RC}$$

$$\therefore q = ce_0 \cdot e^{-t/RC}$$

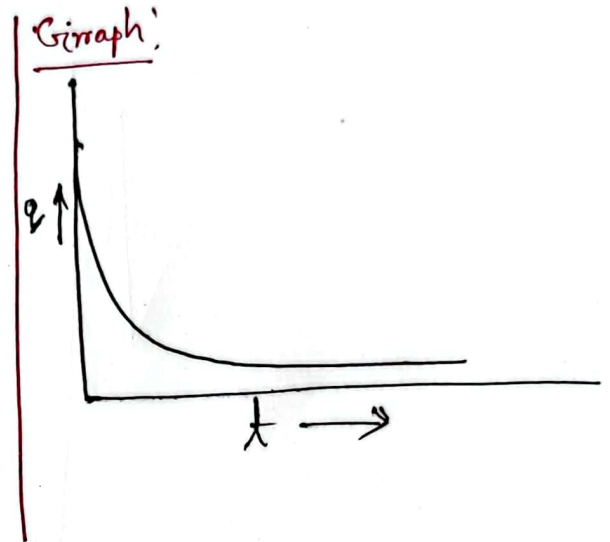

we know,


$$I = \frac{dq}{dt}$$

$$= \frac{d}{dt} (ce_0 \cdot e^{-t/RC})$$

$$= ce_0 \cdot \frac{d}{dt} (e^{-t/RC})$$

$$= ce_0 \cdot e^{-t/RC} \cdot \left(-\frac{1}{RC}\right)$$

$$= -\frac{e}{R} e^{-t/RC}$$

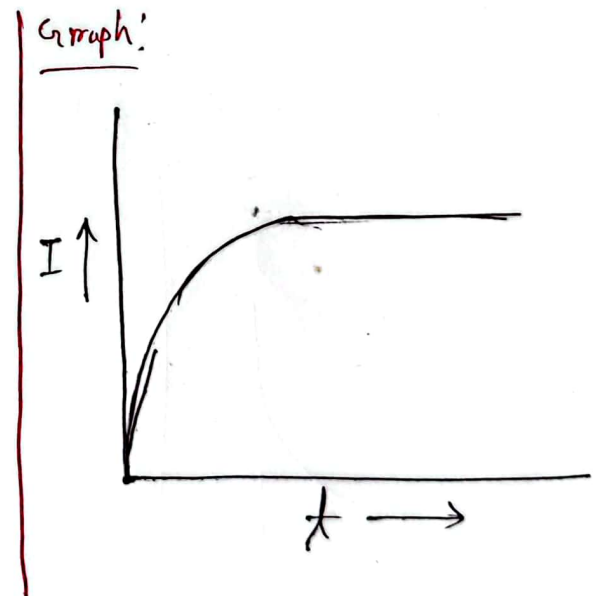

④ Max. current, $I_0 = \frac{e}{R}$